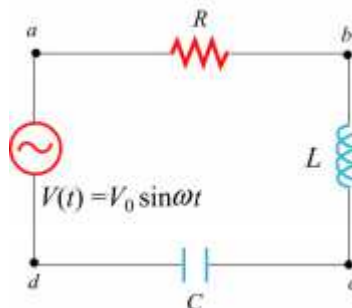


Assignment -2

Module II: Alternating Current Circuits

1. Define the following  
(i) RMS Value (ii) Average Value (iii) Instantaneous Value (iv) Real power (v) Apparent power (vi) Reactive power (vii) Frequency (viii) Balanced three phase circuit
2. A series circuit has  $R=10\Omega$ ,  $L=50\text{mH}$ , and  $C=100\mu\text{F}$  and is supplied with  $200\text{V}$ ,  $50\text{Hz}$ . Find (i) Impedance (ii) current (iii) power (iv) power factor (v) voltage drop across the each element.
3. A coil of resistance  $10\Omega$  and inductance  $0.1\text{H}$  is connected in series with a  $150\mu\text{F}$  capacitor across  $200\text{V}$ ,  $50\text{Hz}$  supply. Calculate (i) Inductive reactance, Capacitance reactance, impedance, current and power factor. (ii) The voltage across the coil and capacitor respectively.
4. A series circuit having pure resistance of  $40\Omega$ , pure inductance of  $50\text{mH}$  and a capacitor is connected across a  $400\text{V}$ ,  $50\text{Hz}$  ac supply. This LC circuit draws a current of  $10\text{A}$ . Calculate (i) Power factor of the circuit, (ii) Capacitor value.
5. Derive the expression for impedance, phase angle, power factor, current, voltage, reactance, apparent power, real power and reactive power for RC series circuit. .
6. Suppose an AC generator with  $V(t) = 150 \sin(100t)$  is connected to a series RLC circuit with  $R = 40.0\Omega$ ,  $L = 80.0\text{mH}$ , and  $C = 50.0\mu\text{F}$



- (a) Calculate  $V_R$ ,  $V_L$ ,  $V_C$  and, the maximum of the voltage drops across each circuit element.
  - (b) Calculate the maximum potential difference across the inductor and the capacitor between point b and d
7. A sinusoidal voltage  $V(t) = 200\sin\omega t$  is applied to a series RLC circuit with  $L=10.0\text{mH}$ ,  $C=100\text{nF}$  and  $R=20.0\Omega$ . Find the following quantities: (a) the resonant frequency, (b) the amplitude of the current at resonance, (c) the quality factor  $Q$  of the circuit, and (d) the amplitude of the voltage across the inductor at the resonant frequency.
  8. A coil of resistance  $10\Omega$  and inductance  $0.1\text{H}$  is connected in series with a  $150\mu\text{F}$  capacitor across a  $200\text{V}$ ,  $50\text{Hz}$  supply. Calculate the voltage across the coil and the capacitor respectively.
  9. A circuit is composed of a resistance  $6\Omega$  and a series capacitive reactance of  $8\Omega$ . A voltage  $E(t)=141 \sin 314t$  is supplied to the circuit. Find (i) Complex impedance, (ii) Effective value of current, (iii) Power delivered to the circuit, (iv) Capacitance of the capacitor.