

Resistances in Series


$R_1 \rightarrow R_n$
 $\rightarrow \text{Max} \rightarrow \text{Min}$
 $V_1 \rightarrow V_n$

$$V = V_1 + V_2$$

$$V = I(R_1 + R_2) + IR$$

$$R = R_1 + R_2$$

Resistances in parallel

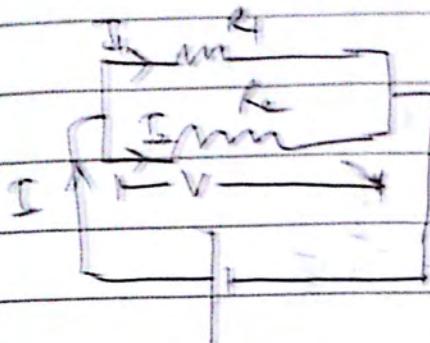

$$I = I_1 + I_2$$


$$I = \frac{V}{R_1} + \frac{V}{R_2}$$

$$\frac{V}{R_{\text{eq}}} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$$

Sources
 ↗ Current source
 ↘ Voltage source

* In current source ideal ~~current~~

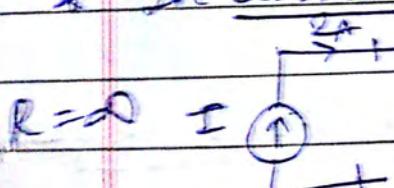

internal impedance is infinite

Practical (Connected in Parallel)



There are losses but not so in ideal

* Voltage Source

Resistance of ideal voltage source

$$\text{Ideal} \quad R = 0$$

$$\frac{V}{R} = 0$$


Internal resistance resistance is connected in series

Prac.

$$V = \frac{E - I R_{se}}{1 + \frac{R_{se}}{R}}$$


$$V - I R_{se} = 4.5$$

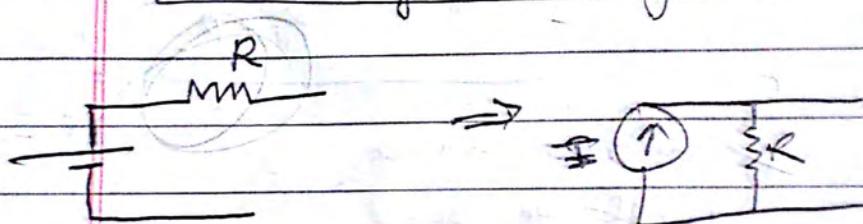Conversion from voltage source to current source



$$I = \frac{V}{R}$$

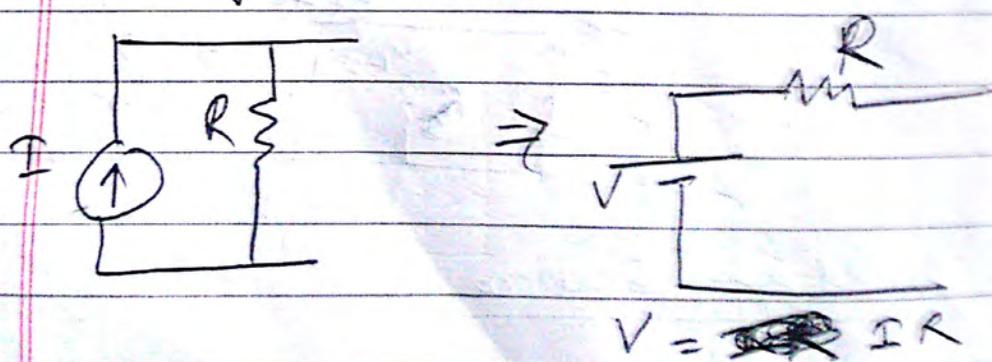
Conversion from current source to voltage source:




D.C \rightarrow Constant value

$$V = 0$$

$$I = 0$$


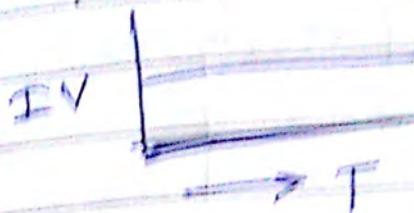


A.C \rightarrow varies with time

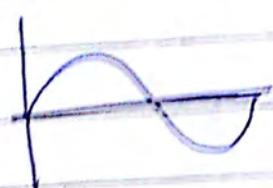


general (sinusoidal)

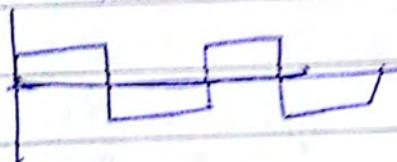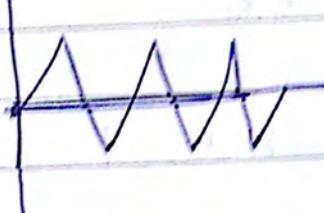Peak sharp \rightarrow losses are more
 \rightarrow as losses are less



\propto No. of loops

$=$ No. of eqⁿ

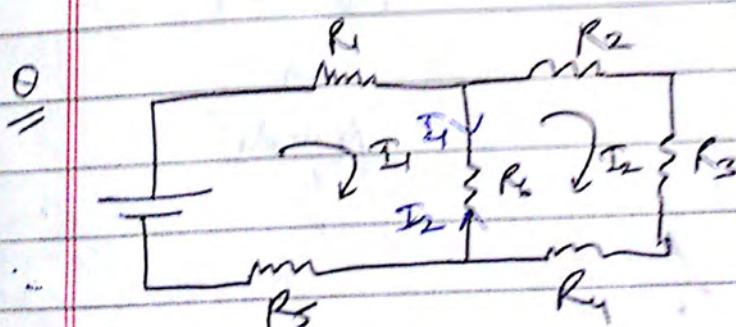

$$R_1 \rightarrow I_1$$

$$R_2 \rightarrow I_2$$


$$R_5 \rightarrow I_1$$

$$R_3 \rightarrow I_2$$

$$R_4 \rightarrow I_2$$

$$R_6 \rightarrow I_1 - I_2$$

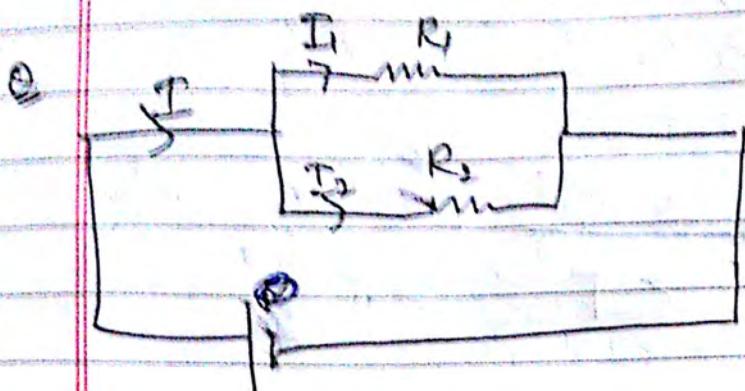
Current divider rule: (Resistances conn. in parallel)



$$I_1 = \frac{IR_2}{R_1 + R_2}$$

$$I_2 = \frac{IR_1}{R_1 + R_2}$$

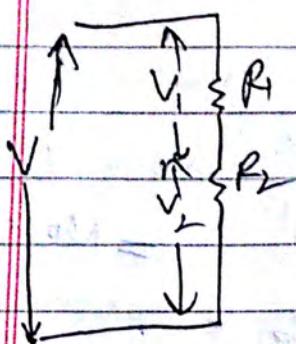Voltage divider rule: { when resistances are connected in series }





$$V_1 = V \frac{R_1}{R_1 + R_2}$$

$$V_2 = V \frac{R_2}{R_1 + R_2}$$

4/1/17

Kirchoff's Voltage Law: { Applied across the loop? }

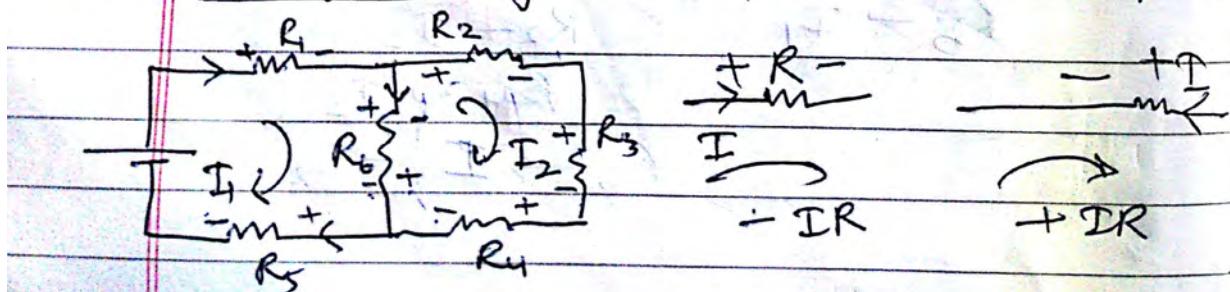

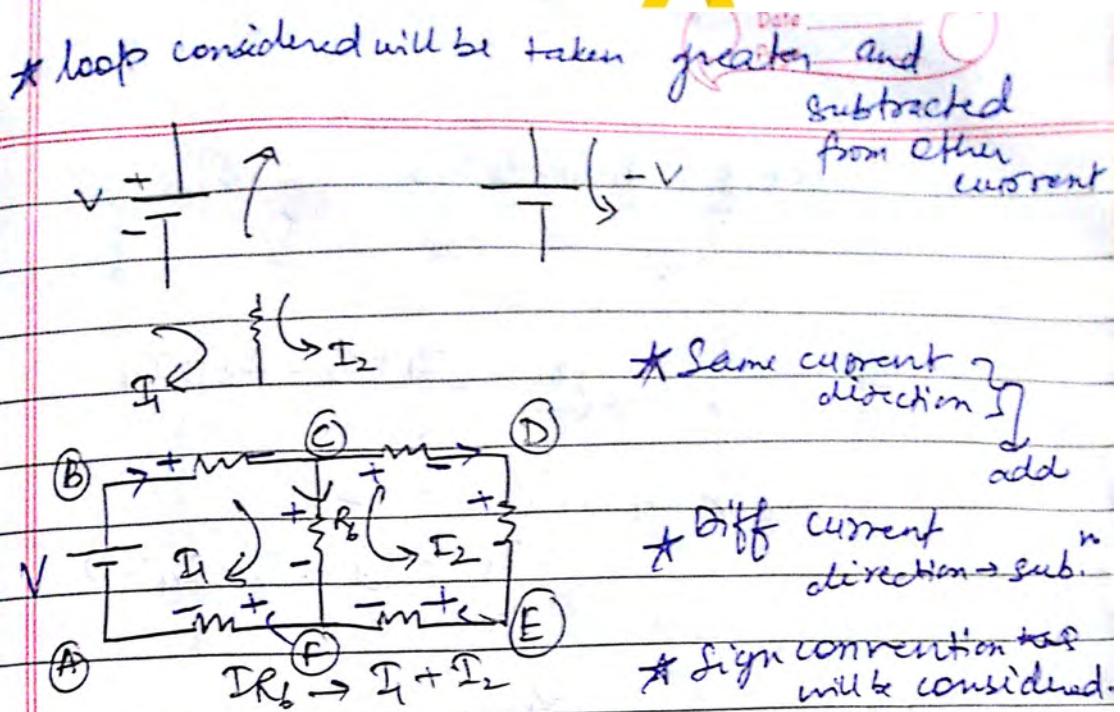


loop I

$$V - I_1 R_1 - (I_1 - I_2) R_6 = 0 \rightarrow (1)$$

loop II
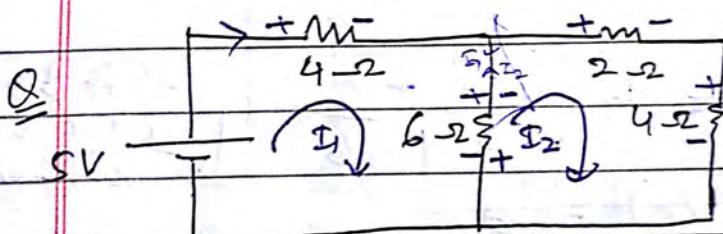
$$-(I_2 - I_1) R_6 - I_2 R_2 - I_2 R_3 - I_2 R_4 = 0 \rightarrow (2)$$



Solⁿ: loop I:

$$5 - I_1 (4) - (I_1 - I_2) 6 = 0$$

$$5 - 10 I_1 + 6 I_2 = 0 \rightarrow (1)$$

loop II,


$$-(I_2 - I_1) 6 - (2 I_2) - 4 (I_2) = 0$$

$$9 I_2 - 6 I_1 = 0$$


$$-12 I_2 + 6 I_1 = 0 \rightarrow (2)$$

$$I_1 = \frac{5}{7} \quad I_2 = \frac{5}{14}$$

Kirchoff's Current Law:

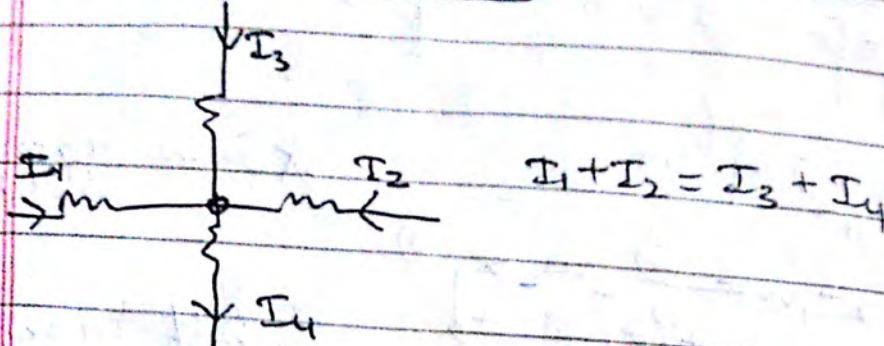

$$I_1 + I_2 - I_3 - I_4 = 0$$

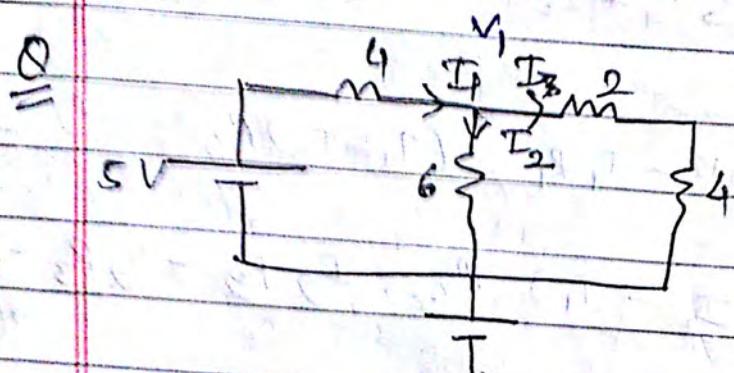

$$I_1 + I_2 + I_3$$

$$\frac{5 - V_1}{4} = \frac{V_1 - 0}{6} + \frac{V_1}{3}$$

[as R1 & R2 are in series]

$$(5 - V_1) = \frac{2V_1}{3}$$

$$15 - 3V_1 = 4V_1$$

$$\frac{15}{7} = V_1$$

~~Eq 1~~

~~$$\frac{5 - 15}{4} = \frac{15}{6} - \frac{30}{42}$$~~

$$I_2 = 5/14$$

$$I_1 = 5/7$$

$$I_3 = 5/14$$

A lower pt is ground pt.

* Give direction of current

* Identify node (same as no. of eq)

Date _____
Page _____

$V \rightarrow$ potential diff.
 $\Sigma V_1 - V_2$




at Node (I) $I_1 = I_2 + I_3$

$$V - V_1 = \frac{V_1 - 0}{R_1} + \frac{V_1 - V_2}{R_2}$$


at Node (II) $I_3 + I_5 = I_4$

$$\frac{V_2 - 0}{R_4} = \frac{V_3 - V_2}{R_5} + \frac{V_1 - V_2}{R_3}$$

Q117 Superposition theorem:

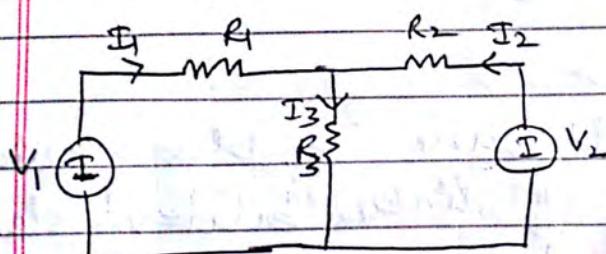


(Assume V_1 acting alone):

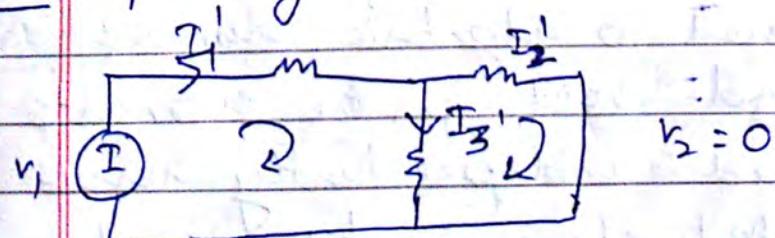


$$I_1' = \frac{V_1}{R_{eq}}$$


$$R_{eq} = R_1 + (R_2 || R_3)$$

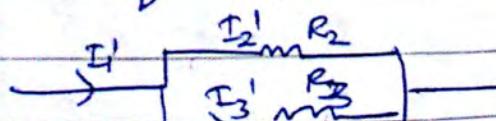

* No of cases: No. of sources

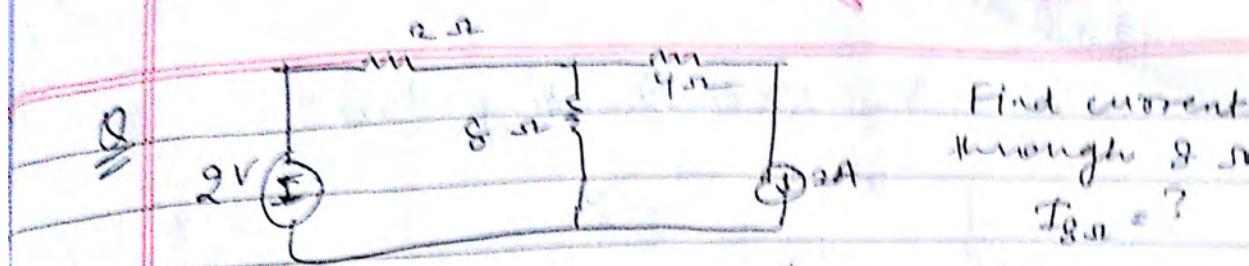


Solⁿ: Case I: 2V acting alone

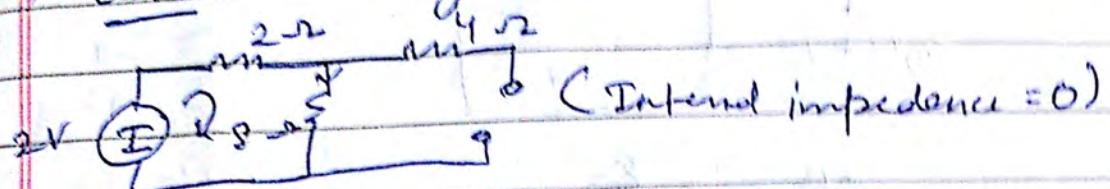


$$I_8 = \frac{2}{8+2} = \frac{1}{5} A$$

Case 2: 2A source is acting


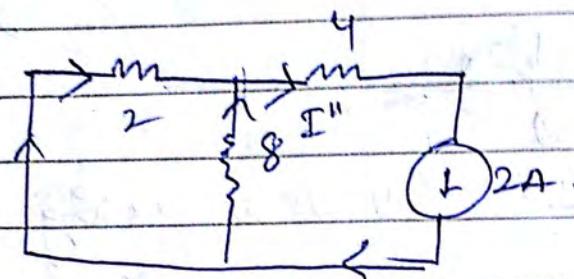


$$\begin{aligned} I'' &= 2 \times 2 \\ I'' &= \frac{2}{10} \\ I'' &= \frac{2}{5} \end{aligned}$$

$$I_{8\Omega} = \frac{1}{3} - \frac{2}{5} = -\frac{1}{5} A \quad \left[\frac{1}{5} \text{ dir.} \right]$$

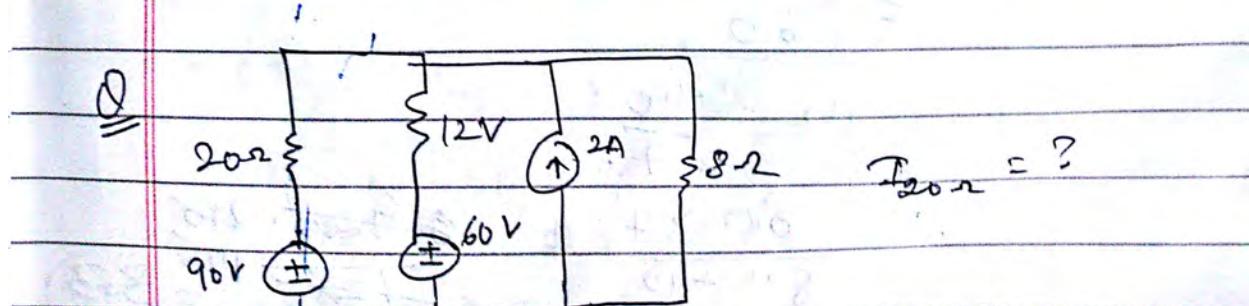

Case I: 90V is acting alone.

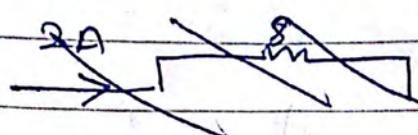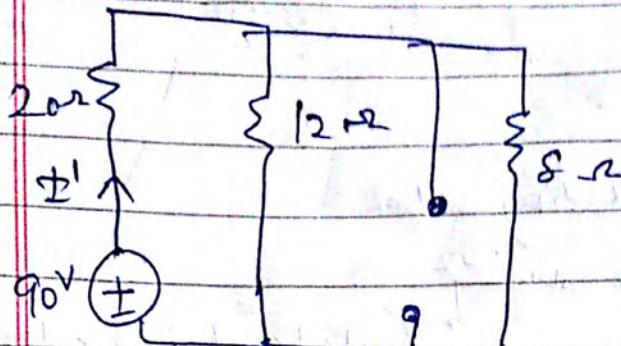


$$I' = \frac{90}{2\Omega + 12\Omega + 8\Omega} = 3.6 \text{ A} \uparrow$$

26

~~= 0.9 A~~

Case II: 60V is acting alone.

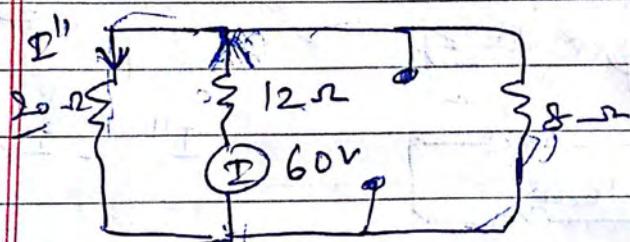

(8x5)

$$I'' = \frac{60}{12\Omega + (2\Omega || 8\Omega)}$$


$$\frac{2 + 5}{40} \Rightarrow \frac{7}{40}$$

$$= \frac{60}{12 + \frac{40}{7}}$$

$$= \frac{60 \times 7}{84 + 40} = \frac{420}{124} = \frac{105}{31} = 3.3$$

62
31


AT

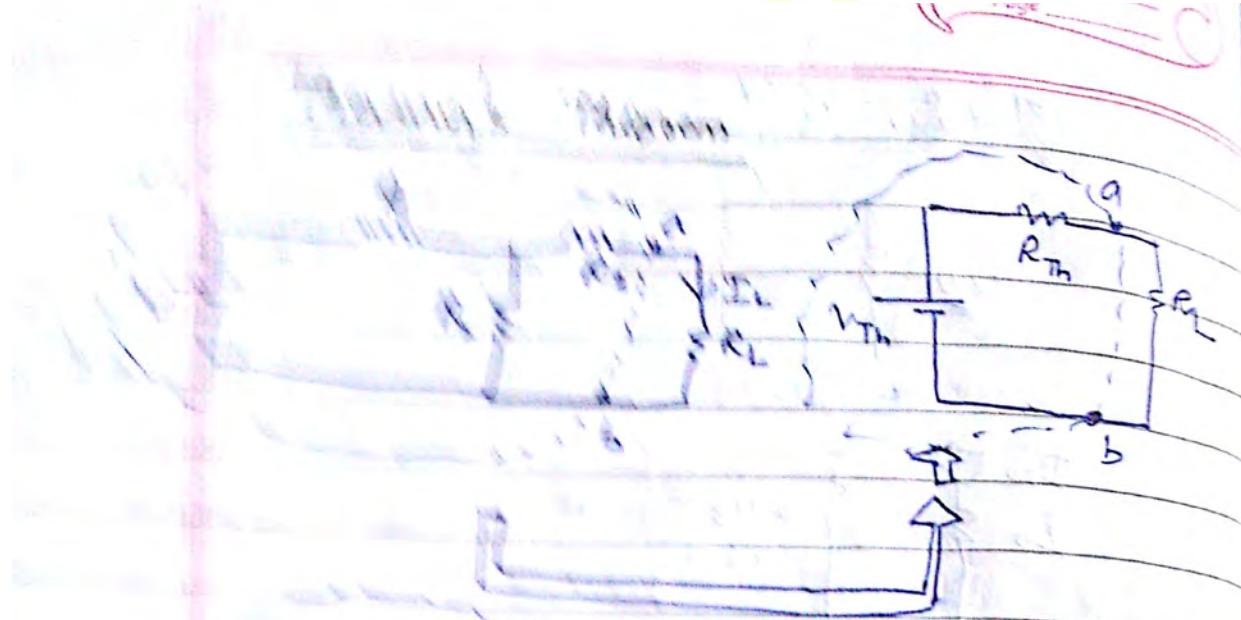


$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$R_{Th} = R_{eq} = \frac{(R_1 || R_2)}{+ R_3}$$


$$V_o = V_m^2 / IR_2$$

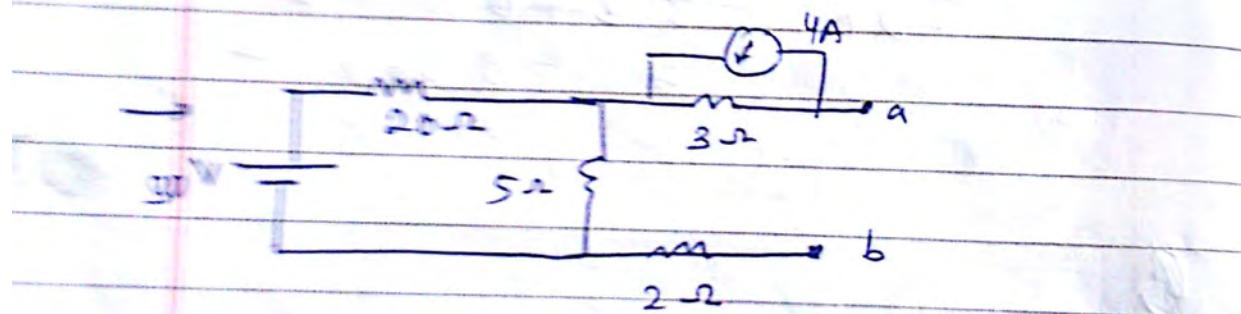

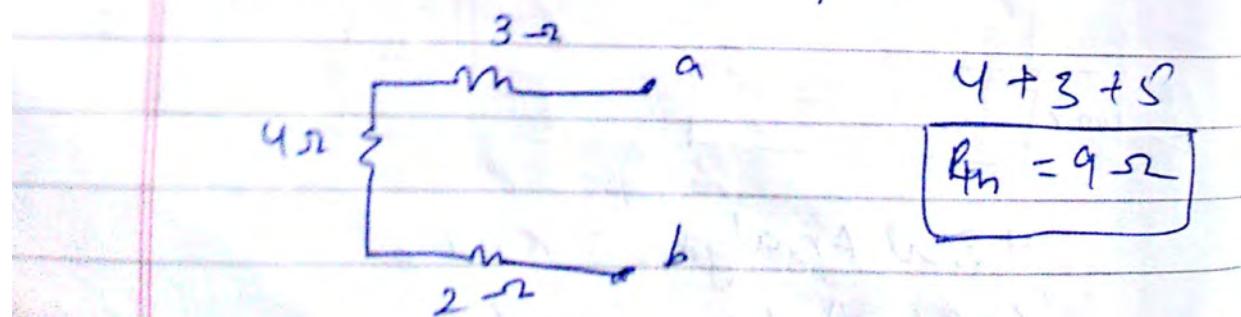Find Thévenin's eq. across point a, b
 voltage source short circuited
 current source is open



$$R_{Th} = 9\Omega$$

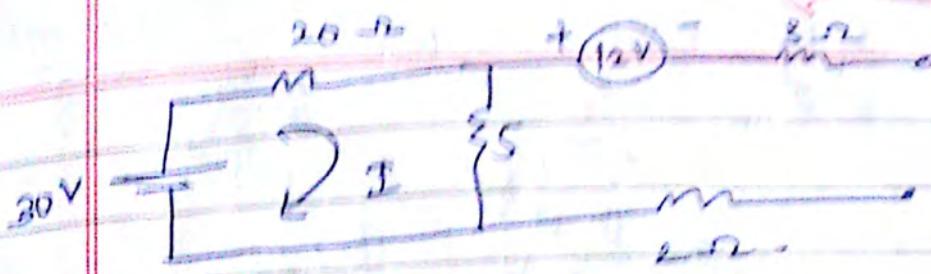


$$I = \frac{30}{25} = 1.2A$$



applying KVL,

$$12 - (1.2 \times 5) + V_{Th} = 0$$

$$V_{Th} = -6$$

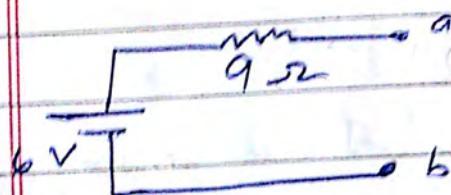


$$I_1 = \frac{6}{9}$$

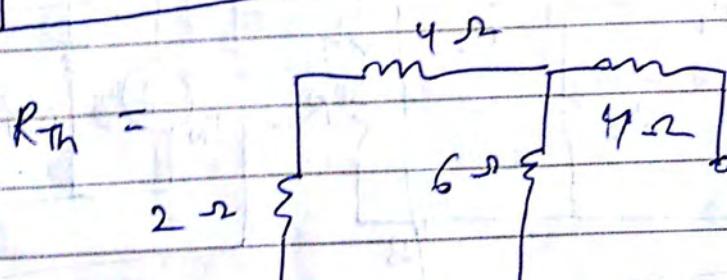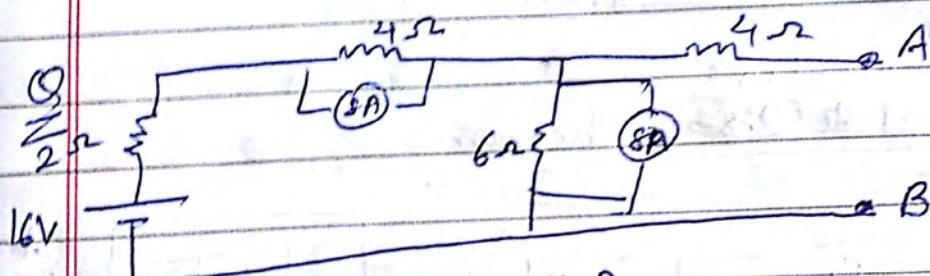

$$R_{Th} = 7$$


max power transf. \rightarrow A

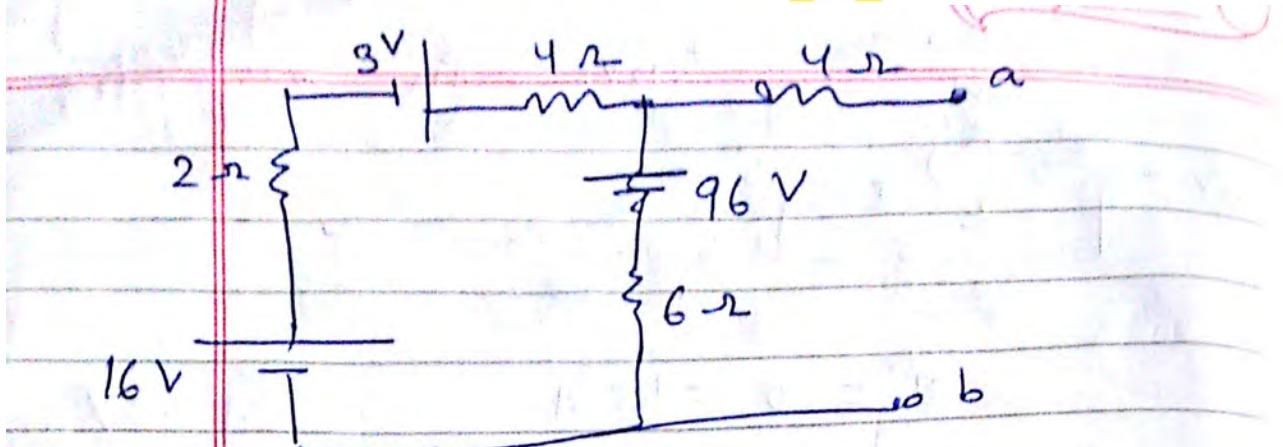


$$16 - 2I + 3I - 4I - 96 - 6I = 0$$
$$I = -4A$$

$$-4 \times 6 + 96 = V_{ab}$$

$$V_{ab} = 72V$$

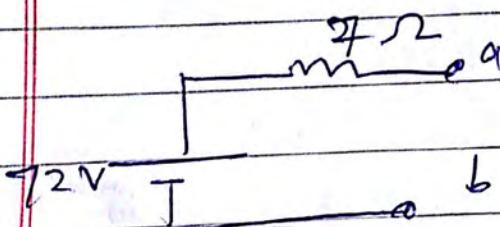

~~16 || 17~~ ~~Norton's~~ ~~Theorem~~ Norton's Theorem:

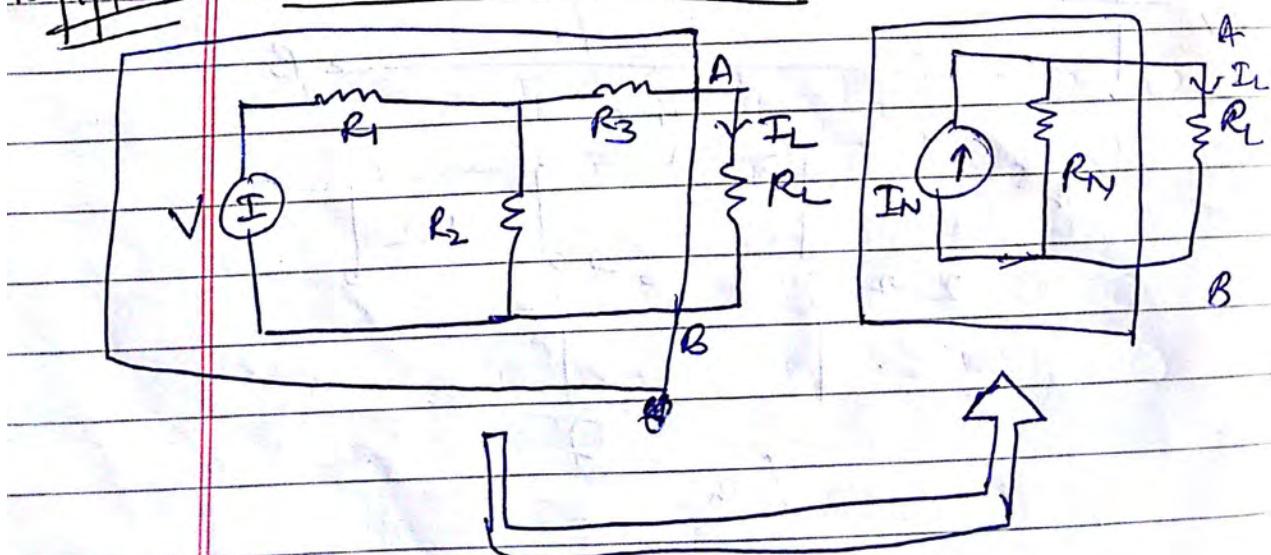

$$I_L = I_N \frac{R_N}{R_N + R_L}$$

$R_N \rightarrow R_{Th}$ (Eq. Resistance)


↓
Same method
SC voltage source

Open circuit load current


$$I_2 = I_{sc} =$$

Step I:

I_N or I_{sc}

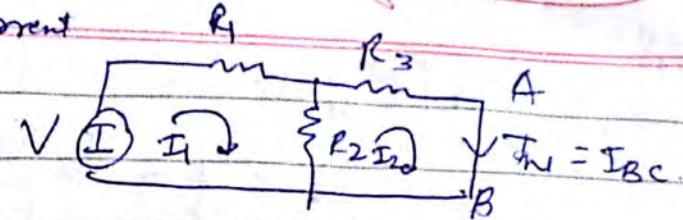

Step II: R_N

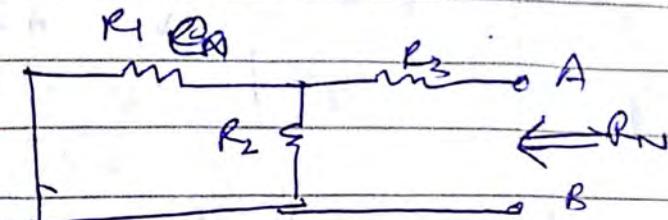

Look from load resp. side


$$(R_1 || R_2) + R_3 = R_N$$

$I_N \rightarrow$

Step Norton's theorem:


Step I: To find I_N / Norton's Current. I_N is short circuit current flowing through the terminal AB.

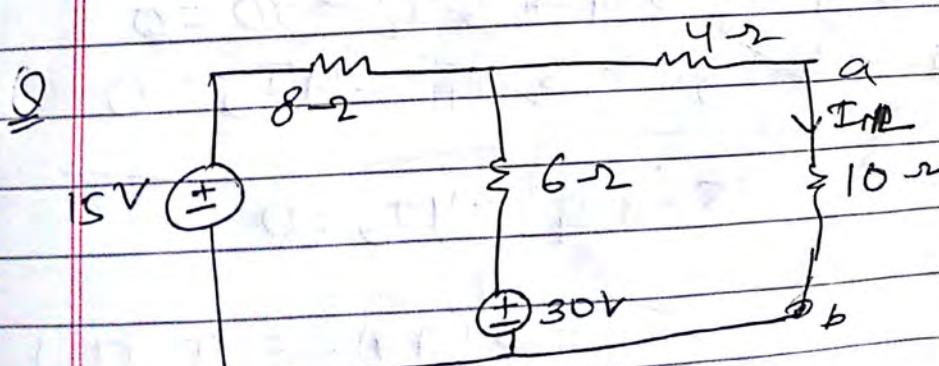Step II: R_N (Norton's Resistance) → called as equivalent resistance. It is found out by short circuiting voltage source and open circuiting current sources (sources replaced by their internal impedance) and load resistance is removed. R_N is viewed from open circuited terminals AB.



Find I_{AB} I_{10} through Norton's theorem.


Soln: $R_N | R_m \Rightarrow$

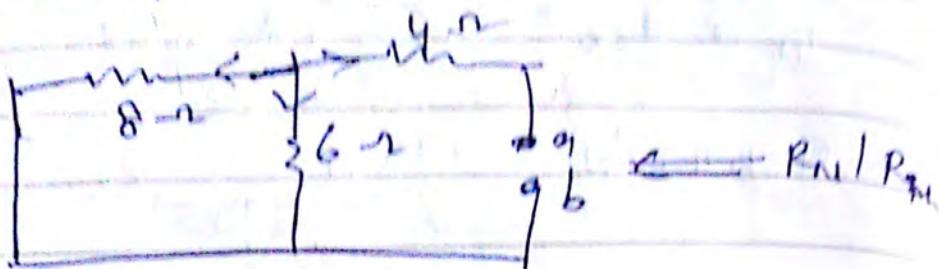

$$R_m = (8 || 6) + 4 \\ = 7.4 \Omega$$

$$V = IR \\ I = \frac{V}{R}$$

$I_N \Rightarrow$

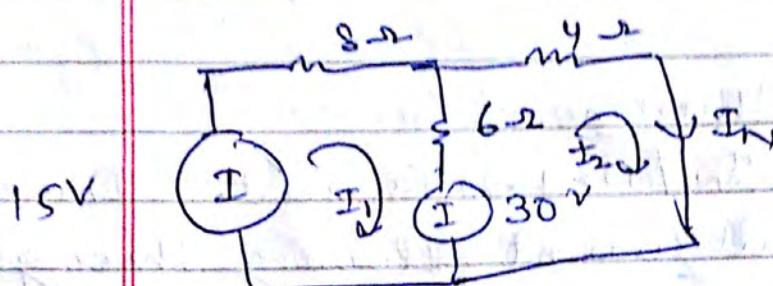

~~$I_2 = I_N (I_{sc}) =$~~

~~at~~

~~$15 - 8(I_1) - 6(I_1 - I_2) - 30 = 0 \\ + 6I_2 - 30 = 0$~~

$$15 - 8I_1 - 6(I_1 - I_2) - 30 = 0 \\ 30 - 6(I_2 - I_1) - 4I_2 = 0$$


~~$15 - 8I_1 - 6I_1 + 6I_2 - 30 = 0$~~

~~$30 - 6I_2 + 6I_1 - 4I_2 = 0$~~

$$15 - 8I_1 - 4I_2 = 0$$

$$I_2 = 3.17 A. = I_N (I_{sc})$$

$$I_1 = 0.288 A.$$

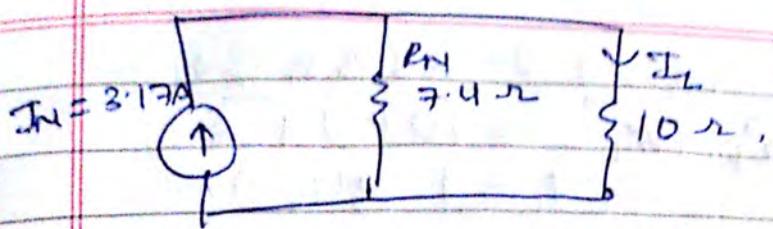


$$I_L = \frac{3.17 \times 7.4}{17.4}$$


$$I_L = 1.35A$$

Therenin's Theorem:

V_{Th} in series with R_{Th}

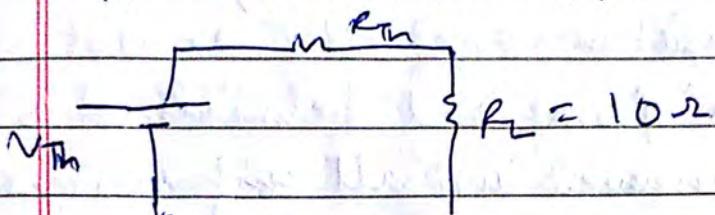

Open circuit load res to find V_{Th} .

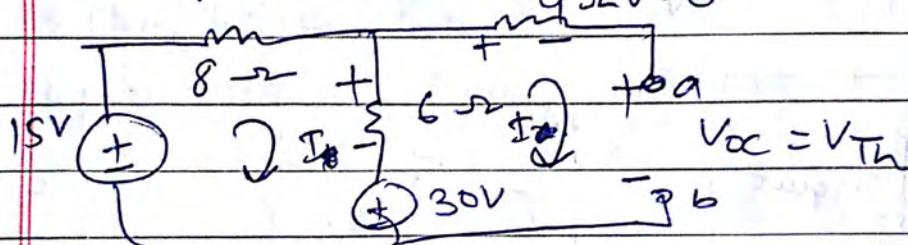

~~$-8I_B - 6(I_B - I_2) + 15 = 0$~~


$$I = \frac{15 - 30}{14} = -1.07A$$

$$30 + 6I - V_{ab} = 0$$

$$V_{ab} = V_{oc} = V_{th} = \frac{23.58}{36.43}$$

~~$I_L = 23.58$~~

Put value in ⁺⁶ Therenin's Circuit.

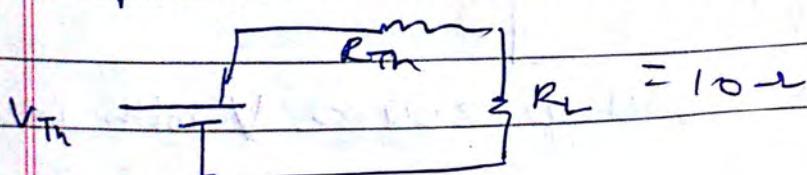


$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{23.58}{70 + 74} \\ I_L = 1.348 \text{ A}$$

~~wh/13~~


~~Max Power Transfer theorem:~~

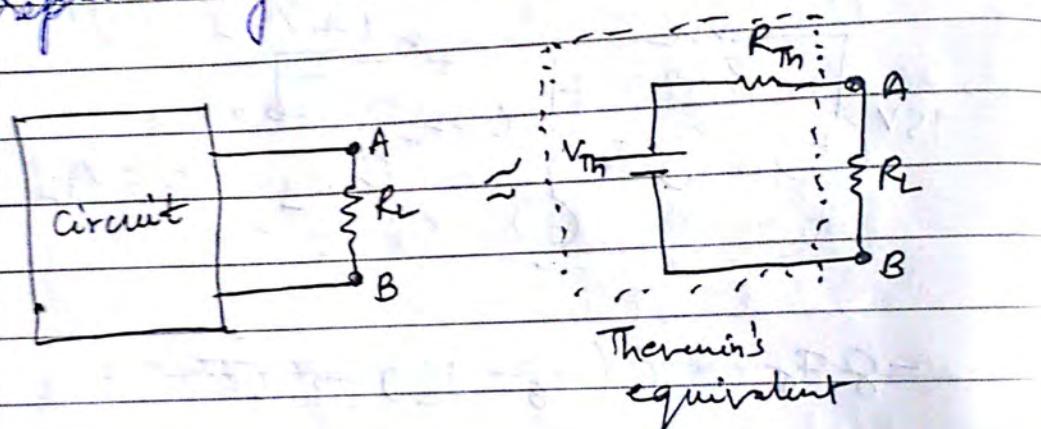In DC circuits, maximum power is transferred from source to load when load resistance is equal to internal resistance of the circuit as viewed from load terminals with load removed and all emf sources replaced by their internal resistances.



$$R_L = R_{Th} \quad (\text{or internal resistance of the circuit})$$

~~Proof:~~

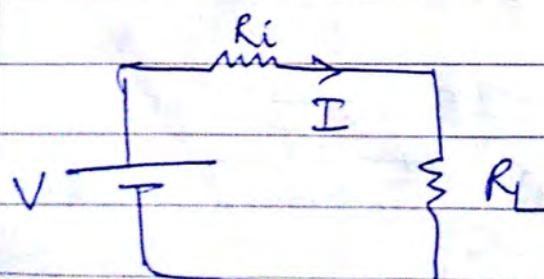

Consider voltage source V with internal

resistance R_i delivering power to load R_L

$$\text{Then } \star, I = \frac{V}{R_i + R_L} \rightarrow \textcircled{1}$$

$$\text{Power delivered, } P = I^2 R_L \rightarrow \textcircled{2}$$

Putting $\textcircled{1}$ in $\textcircled{2}$

$$P = \frac{(V)^2}{(R_i + R_L)^2} R_L$$

As V and R_i are constant

P depends on R_L . \therefore Differentiating P w.r.t R_L , we can get condition for P_{\max} .

$$\frac{dP}{dR_L} = 0 \star$$

$$V^2 \left[\frac{(R_L + R_i)^2 - 2 R_L (R_i + R_L)}{(R_i + R_L)^2} \right] = 0$$

So num. $\star = 0$.

$$(R_L + R_i)^2 - 2 R_L (R_i + R_L) = 0$$

$$\Rightarrow (R_L + R_i)^2 = 2 R_L R_i + 2 R_L^2$$

$$R_L^2 + R_i^2 + 2 R_L R_i = 2 R_L R_i + 2 R_L^2$$

$$R_i^2 - R_L^2 = 0$$

$$(R_i + R_L)(R_i - R_L) = 0$$

Cannot
be 0.

$$R_i + R_L \neq 0 \quad R_i + R_L = 0$$

$$\therefore R_i - R_L = 0$$

$$\Rightarrow R_i = R_L$$

or $R_L = R_i$

Points to be noted:

- ① Efficiency: The circuit efficiency at maximum power transfer is only 50% as one half of the total power is dissipated in internal resist. R_i of the source.

$$\eta = \frac{\text{O/P power}}{\text{I/P power}} = \frac{I^2 R_L}{I^2 (R_i + R_L)}$$

For max. power

$$\therefore R_i = R_L$$

$$\therefore \eta = \frac{1}{2} = 50\%$$

- ② Load voltage: (For max power)

$$V_L = I R_L = \frac{V}{R_i + R_L} \cdot R_L = \frac{V}{2}$$

$V \rightarrow$ supply voltage

- ③ Max. power: (For max.).

Numerical
+ Theory


$$P_{\max} = I^2 R_L$$

$$= \left(\frac{V}{R_i + R_L} \right)^2 \times R_L$$

$P_{\max} = \frac{V^2}{4R_L}$

$V \rightarrow$ Thvenin's voltage

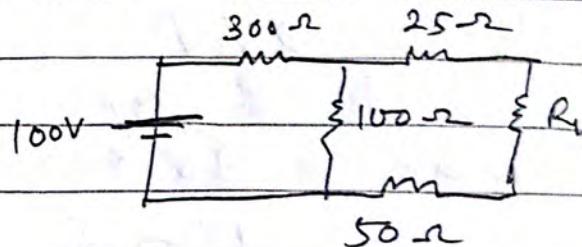
Q Find the maxi. value of R_L necessary to obtain obtain max. power in R_L . Also find the max. power in R_L



$$R_L = ? \quad P_{\max} = ?$$

Solⁿ: Acc. to Max. Power transfer theorem (M.P.T theorem)

$$R_L = R_{Th}$$

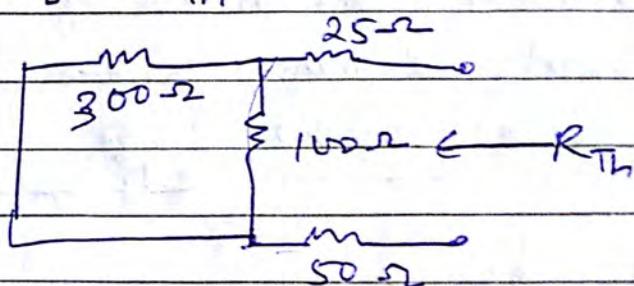


$$\begin{aligned} R_{Th} &= (300 // 100) + 25 + 50 \\ &= 75 + 25 + 50 \\ &= 150 \Omega \end{aligned}$$

∴ Value of $R_L = 150 \Omega$ for M.P.T

$$P_{\max} = \frac{V_{Th}^2}{4R_L}$$

$$= \frac{V_{Th}^2}{4R_L}$$

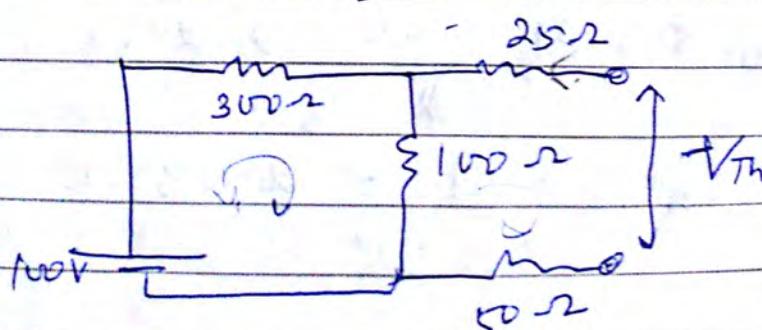

$$V_{Th} = \text{voltage across } 100\Omega \text{ resistor}$$


$$= \frac{100}{400} \times 100$$

$$V_{Th} = 25 \text{ V.}$$


$$P_{max} = \frac{\cancel{25} \times 25}{4 \times \cancel{150}} = \frac{25}{6 \times 4}$$

$$= 1.04 \text{ W}$$

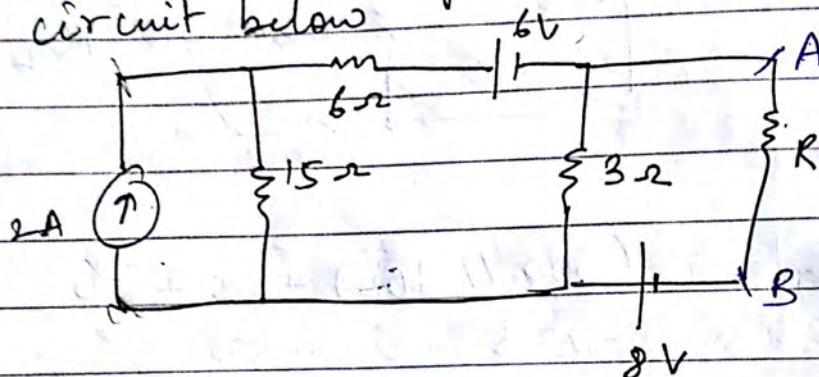Q Calculate the value of R which will absorb maximum power from the circuit below




sol'n: $R = ?$

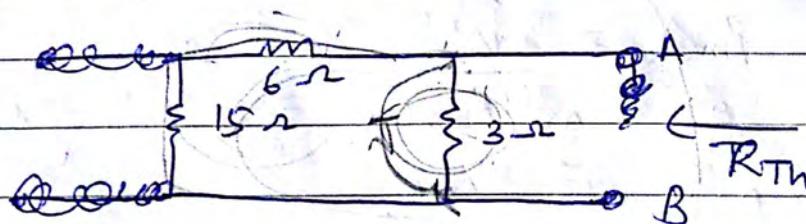



Q ~~21~~ $\frac{1+7}{21} \rightarrow \frac{21}{8}$

$$R_{Th} = R = \frac{21}{8} = 2.63 \Omega$$

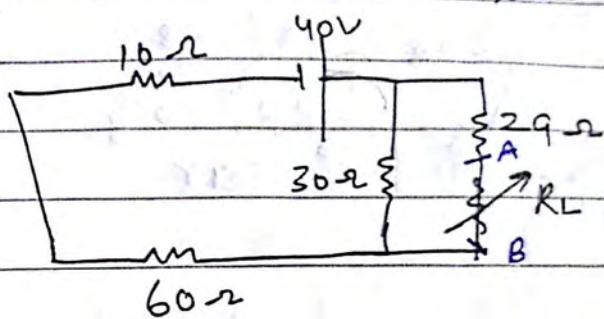Q find the value of R_L for which power transfer is maximum. Also calculate this power.



Solⁿ:

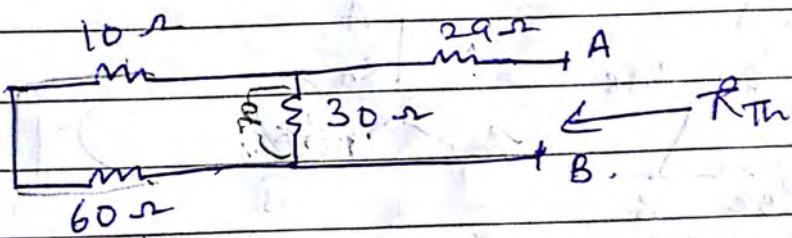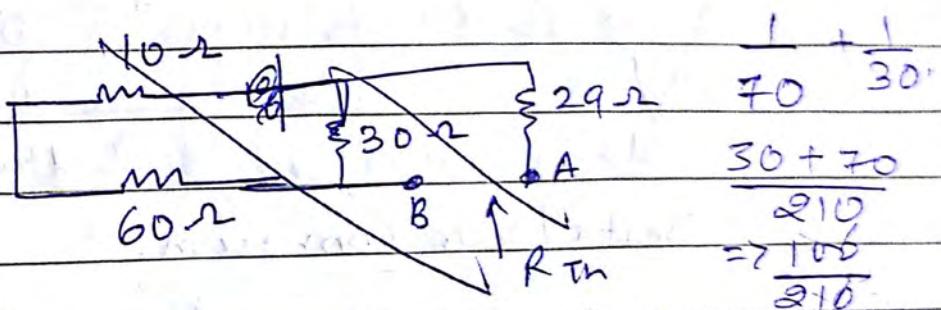

$$R = R_{Th} = 2.1 + 29 \\ = 31.1 \Omega$$

$$\begin{aligned} P_{max} &= \frac{V^2}{4R_{Th}} \\ &= \frac{(40)^2(40)}{4(31.1)} \\ &= \frac{1600}{31.1} \\ &= 51.2 \end{aligned}$$

$$+10I \quad V = IR$$



$$10I +$$

* eq. Res in Δ = $cq \cdot R$


23/11/17

(5M) sub.

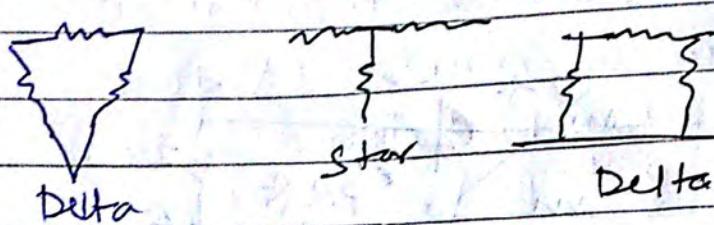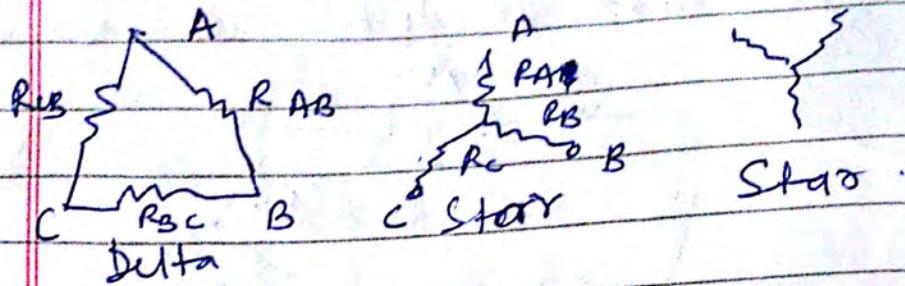Delta / Star & Star / Delta Transformation



Delta / Star Conversion:

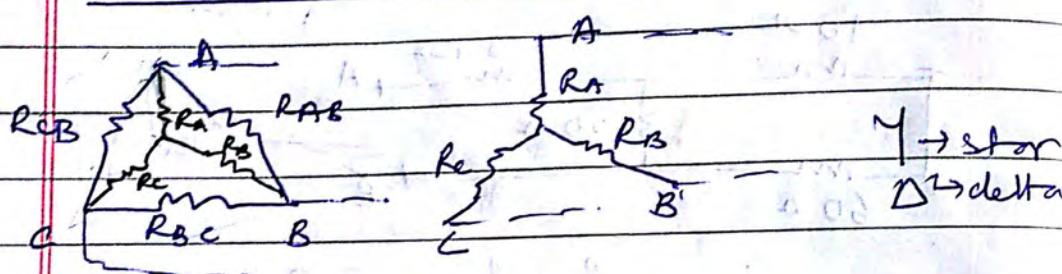

$$A \& B \text{ in } \Delta = R_A + R_B = R_{AB} \parallel (R_{BC} + R_{AC})$$

$$\frac{A \& B \text{ in } \Delta}{R_A + R_B} = \frac{R_{AB}}{R_{AB} + R_{BC} + R_{AC}} \rightarrow ①$$

$$B \& C \text{ in } \Delta = B \& C \text{ in } \Delta$$

$$\frac{B \& C \text{ in } \Delta}{R_B + R_C} = \frac{(R_{AB} + R_{AC})}{R_{AB} + R_{BC} + R_{AC}} \rightarrow ②$$

$$\frac{C \& A \text{ in } \Delta}{R_C + R_A} = \frac{R_{AC} (R_{AB} + R_{BC})}{R_{AB} + R_{BC} + R_{AC}} \rightarrow ③$$

Subtract ② from ① and add to ③

$$R_A = \frac{R_{AB} R_{CA}}{R_{AB} + R_{BC} + R_{CA}} \rightarrow (4)$$

$$R_B = \frac{R_{BC} R_{AB}}{R_{AB} + R_{BC} + R_{CA}} \rightarrow (5)$$

$$R_C = \frac{R_{CA} R_{BC}}{R_{AB} + R_{BC} + R_{CA}} \rightarrow (6)$$

Any arm of Δ star connection =
 product of 2 adjacent arms of Δ
 sum of arms of Δ

Star / Delta conversion:

divide (4) by (5)

$$\frac{R_A}{R_B} = \frac{R_{CA}}{R_{BC}}$$

$$R_{CA} = \frac{R_A R_{BC}}{R_B}$$

divide (4) by (6)

$$\frac{R_A}{R_C} = \frac{R_{AB}}{R_{BC}}$$

$$R_{AB} = \frac{R_A R_C}{R_B}$$


Put in
④

$$R_{BC} = R_B + R_C + \frac{R_B R_C}{R_A}$$

Similarly


$$R_{CA} = R_C + R_A + \frac{R_C R_A}{R_B}$$
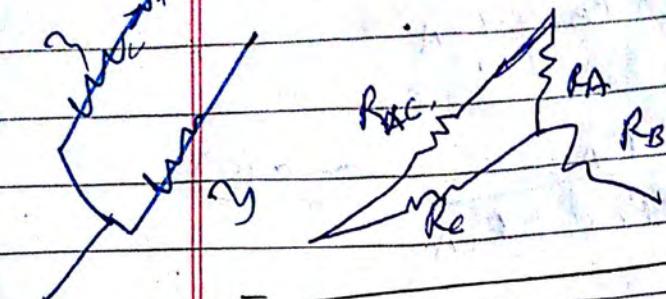
$$R_{AB} = R_A + R_B + \frac{R_A R_B}{R_C}$$



Resistance b/w 2 terminals of Δ =
 Sum of Y resistances connected to
 those terminals + (Product of same
 2 resistances R_A / R_B / 3rd \star or star resistance)

(Q)

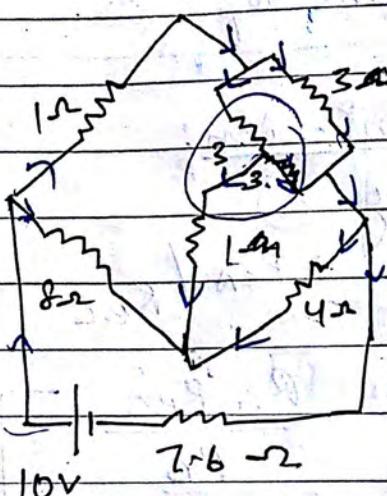

find the value of
 current supplied by
 the battery
 by using star
 delta transform.



Sol'n:



$$R_{AB} = 3 + 3 + \frac{(3 \times 3)}{1} = 15 \Omega$$

$$R_{BC} = 3 + 1 + \frac{3 \times 1}{3} = 5 \Omega$$
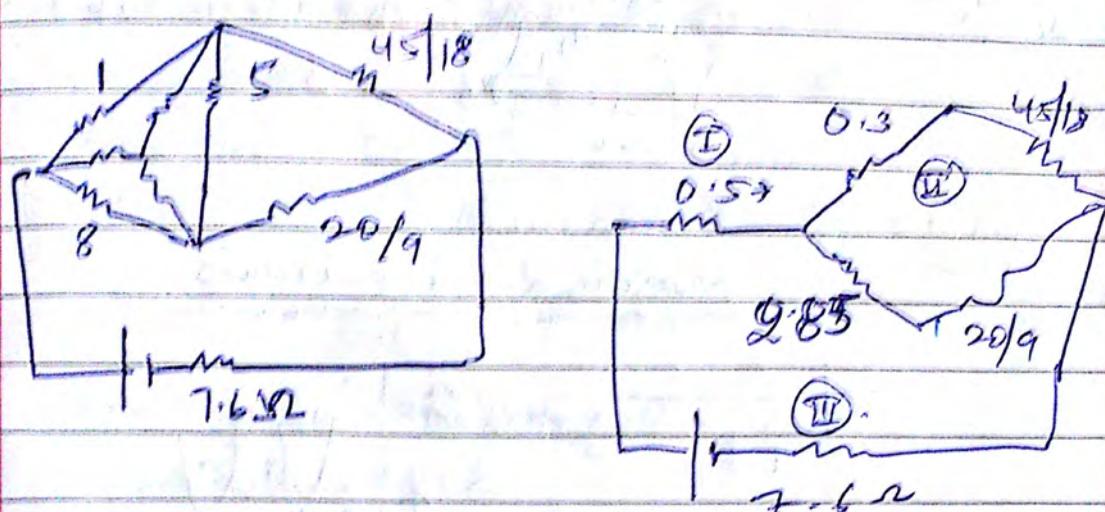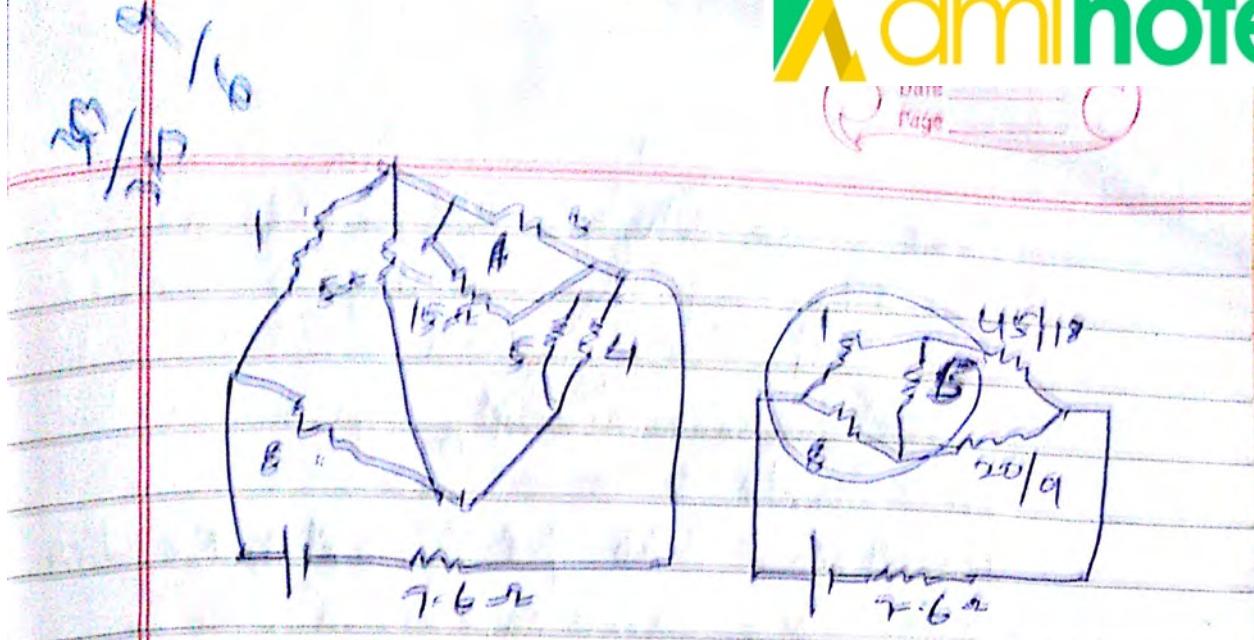
$$R_{CA} = 3 + 1 + \frac{3 \times 1}{3} = 5 \Omega$$



$$R_{eq} \quad R_{II} = \frac{0.3 + 45}{18} \parallel 2.85 + \frac{20}{9},$$

$$= \frac{0.3}{2.8} + \frac{45}{5.02}, \\ \cancel{= 0.55} \approx 4.8$$


$$R_{eq} = 0.57 + \cancel{0.55} = 7.6 + 4.8 \\ = 9.9 \approx 10 \Omega.$$

$$V = D^2$$

$$I = \frac{10}{10} = 1A \text{ (approx)}$$

3 = 121.5

(Q)

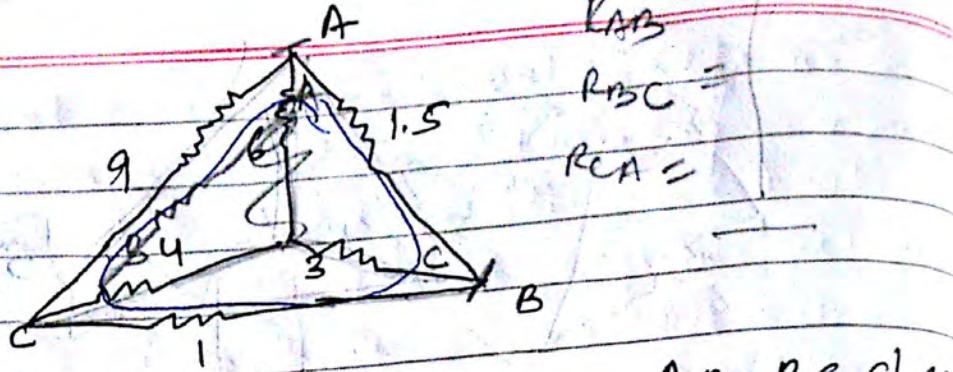

R_{AB}


$R_{BC} =$

$R_{CA} =$

Find req b/w pt- 6 $AB, BC \& CA$

$R_A = 6$

Solⁿ:

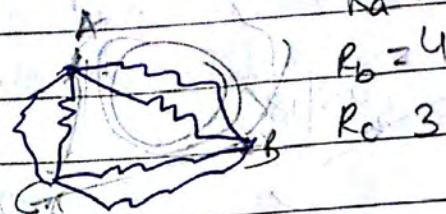

$R_B = 4$

$R_C = 3$

25/11/17

Module 2: A.C. Circuits:

$$v_i | \quad t$$

de

$$v_i | \quad t$$

$\leftarrow T \rightarrow$ ac

$$e = -\frac{d\phi}{dt}$$


(-ive due to Lenz's law & emf generated will oppose cause of motion?)



$$\theta = \omega t, \quad \omega = 2\pi f \text{ (rad/sec.)}$$

$$= 2\pi ft = 2\pi \left(\frac{1}{T}\right) t$$
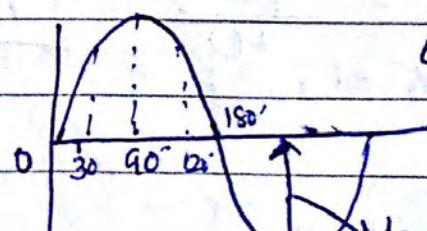
$$f = \frac{1}{T} \rightarrow \text{sec}^{-1} \text{ or Hz}$$



$$e = Blv \sin \theta$$

peak value
max. value

your
form
am

$$V_i = V_m \sin \omega t_1$$

$$V_0 = V_m \sin \omega t_2$$

$$\text{or } V_m \sin \theta = 0$$

$$\text{or } V_m \sin 2\pi f t_2$$

$$\text{or } V_m \sin \frac{2\pi}{T} t_2$$

$$\theta = 2\pi f t = \omega t$$

NG
CC
S C.I.

value that

Instantaneous value: Changes from time to time

e. ~~Average~~ value

o Peak value / Max value


e. Average value: Area under curve

Interval
of curve

[but 0

in case
of sinusoidal
wave]

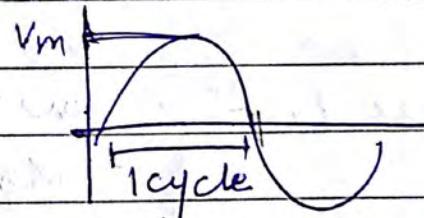Only calculate avg. value of one cycle in case
of sinusoidal wave



Integrate V_m to get area under the
curve

$$\Delta A = \int_0^T V_m \sin \omega t \quad [\text{for full cycle}]$$

* Max value is also called amplitude of
the wave form. Highest value

* Avg. value = Net area under curve
for time 't'

time 't'

Root mean square (RMS): Effective or root value of an alternating current is that steady state (D.C.) which when flowing through a given resistance for a given time produces same amount of heat as produced by alternating current when flowing through the same resistance for the same time.

Factors:

$$\textcircled{1} \quad \text{From factors: } \frac{\text{RMS value}}{\text{Avg. value}}$$


$$\textcircled{2} \quad \text{Peak factor: } \frac{\text{max. value}}{\text{RMS value}}$$

To find RMS value for sinusoidal value:

(1) Find avg. value ~~mean value~~

(2) Take Square

(3) Take Root I_{RMS}

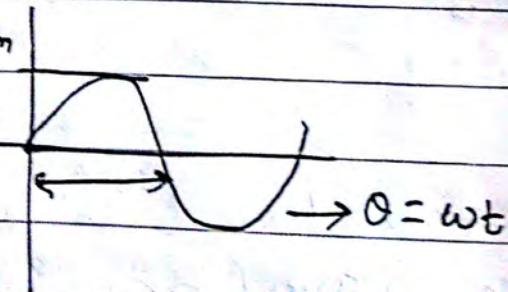

~~avg. value~~ $\int id\theta$

$$i = I_{\text{m}} \sin \theta$$

$$= \int_0^\pi I_m \sin \theta d\theta$$

~~sine value~~ = ~~$\int_0^\pi I_m^2 \sin^2 \theta d\theta$~~

$$= I_m \int_0^\pi \sin^2 \theta d\theta$$

~~sine value~~ = ~~$\sqrt{\int_0^\pi I_m^2 \sin^2 \theta d\theta}$~~

$$= \sqrt{I_m^2 \int_0^\pi \sin^2 \theta d\theta}$$

$$= \frac{I_m}{\sqrt{2}}$$

~~sine value~~ = $0.707 I_m = I_{rms}$

avg. value = $\frac{2 I_m}{\pi}$

$I_{avg} = 0.637 I_m$


Form factor = $\frac{0.707 I_m}{0.637 I_m} = 1.11$

Peak factor = $\frac{I_m}{0.707 I_m} = 1.41$

also called
as crest
factor

11/17

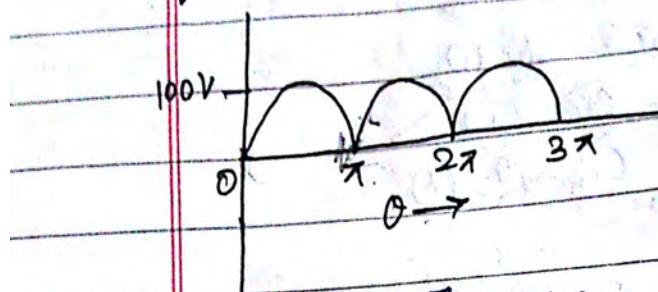Q Find rms value, avg. value & form factor of wave form given:



Solⁿ: $V_{av} = \frac{1}{\pi} \int_0^\pi v(\theta) d\theta$

$$v(\theta) = V_m \sin \theta$$

$$V_{av} = \frac{1}{\pi} \int_0^\pi V_m \sin \theta d\theta$$

$$V_{av} = \frac{1}{\pi} \int_0^\pi V_m \sin \theta d\theta$$

$$= \frac{1}{\pi} \left[-V_m \cos \theta \right]_0^\pi$$

$$= -\frac{100}{\pi} [-2]$$

$$V_{av} = \frac{200}{\pi}$$

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_0^\pi v^2(\theta) d\theta}$$



$$v(\theta) = V_m \sin \theta$$

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_0^\pi V_m^2 \sin^2 \theta d\theta}$$

$$= \sqrt{\frac{1}{2} \int_0^{\pi} (100)^2 \sin^2 \theta d\theta}$$

$$= (100) \sqrt{\frac{1}{2} \int_0^{\pi} 1 - \cos 2\theta d\theta}$$
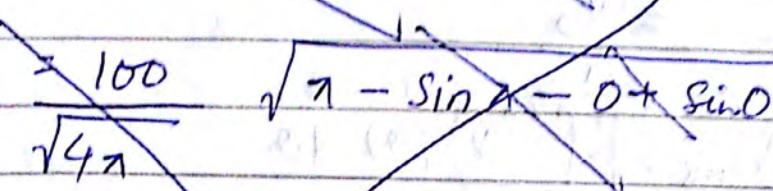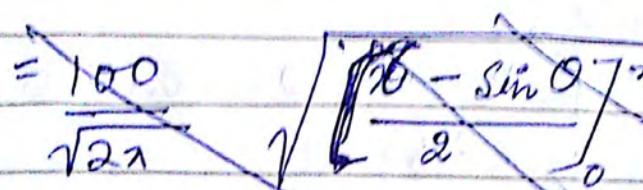
$$= 700 \sqrt{1 - \cos(2\pi)} = 0 + \cancel{100\pi}$$



$$= \frac{100}{2\sqrt{2}}$$


$$= \frac{100}{2} = 50$$

$$V_{rms} = \frac{100}{\sqrt{2}}$$

$$F.F = \frac{Rms}{Avg.} = \frac{100/\sqrt{2}}{200/\pi} = 1.11$$

$$P.F = \frac{100}{\text{max.}} = \frac{100}{100/\sqrt{2}} = \sqrt{2} = 1.414$$

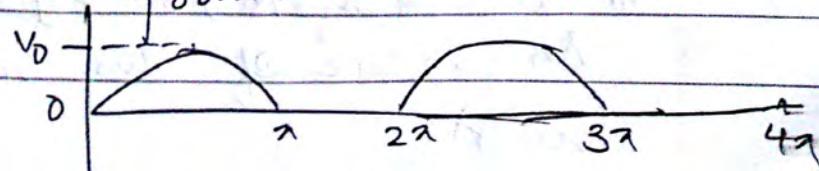Q. Find avg. value, rms value & f.f of given wave form:



→ Here $0 \rightarrow 2\pi$ is complete cycle

$$\text{Soln: } \text{Avg } V_{\text{avg}} = \frac{1}{2\pi} \int_0^{2\pi} v(\theta) d\theta$$

$$v(\theta) = \frac{V_0 \sin \theta}{2\pi} \quad (0 \text{ to } \pi) \\ = 0 \quad (\pi \text{ to } 2\pi)$$

$$V_{\text{avg}} = \frac{1}{2\pi} \int_0^{2\pi} V_0 \sin \theta + 0 d\theta \\ = \frac{V_0}{2}$$

$$V_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v^2(\theta) d\theta} \\ = \sqrt{\frac{\int_0^{2\pi} V_0^2 \sin^2 \theta d\theta}{2\pi}}$$


$$= \frac{V_0}{\sqrt{2}}$$

$$F.F = \frac{V_{\text{rms}}}{V_{\text{avg}}} = \frac{V_0/\sqrt{2}}{V_0/2} = \sqrt{2}/2$$

$$P.F \text{ (crest factor)} = \sqrt{2} = \frac{V_0}{V_0/\sqrt{2}} = \sqrt{2}$$

* In rectangular wave form $P.F = F.F = 1$
 (as all values are const.) and let
 max. length = A, so avg. value &
 rms value of this wave form
 is A

100 + 100 = 200

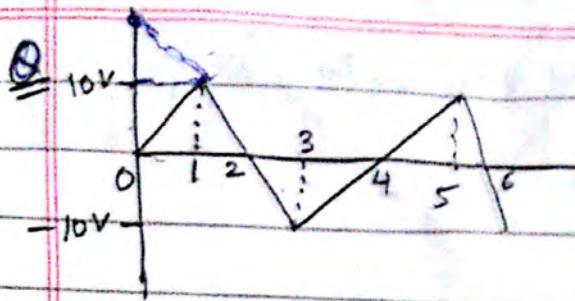

(2, 0)

$$0 = -10 \times 2 + C$$

$$\Rightarrow C = 20$$

$$v_{avg} = \frac{\frac{1}{2} \times 2 \times 10}{2} = 5$$

~~Ansatz~~

$$V_{rms} = \sqrt{\frac{\int_0^2 v^2(t) dt}{2}} = \sqrt{\frac{\int_0^1 (10t)^2 dt + \int_1^2 (-10t + 20)^2 dt}{2}}$$

$$C = \left[\frac{100t^3}{3} \right]_0^1 + \left[-\frac{10t^2}{2} + 20t \right]$$

~~Check~~

$$= \frac{100}{3} + \left[\frac{100t^3}{3} + 400t - \frac{200t^2}{2} \right]_0^1$$

$$= \frac{100}{3} + \left[\frac{800}{3} - \frac{100}{3} + 400 - 100 - \frac{800}{2} + \frac{200}{2} \right]$$

$$= \frac{100}{3} \left[\frac{300}{3} + \frac{700}{3} - 630 \right]$$

$$= \frac{1000}{3 \times 2}$$


$$= \sqrt{\frac{1000}{6}} = 5773V$$

$$V_{rms} = 5.773V$$

$$F.F = \frac{V_{rms}}{Avg} = \frac{5.733}{5} = 1.154$$

2/17

A.C. through resistance

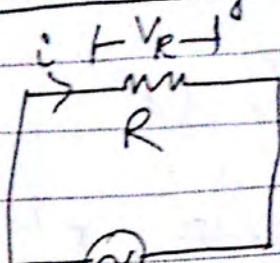


$$V = V_m \sin \omega t \rightarrow ①$$

$$i = \frac{V}{R}$$

$$= \frac{V_m \sin \omega t}{R}$$

$$i = I_m \sin \omega t \rightarrow ②$$

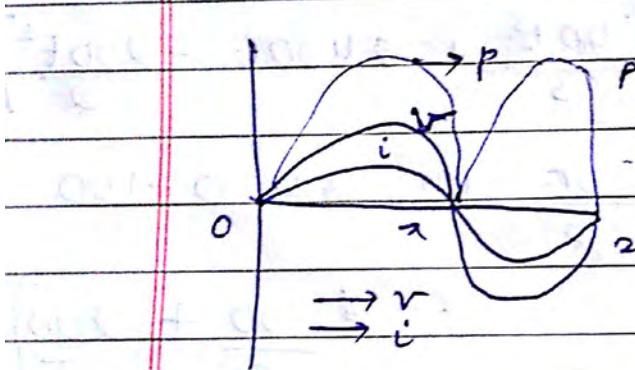

$$P = VI$$

$$= V_m \sin \omega t \cdot I_m \sin \omega t$$

$$= V_m I_m \sin^2 \omega t$$

$$= I_m V_m / \left(1 - \cos 2\omega t \right)$$

$$= \frac{V_m I_m}{2} - \frac{V_m I_m \cos 2\omega t}{2}$$

avg. power = true power = active power

$$= \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m}{2} - \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m \cos 2\omega t}{2}$$


~~cancel~~

$$= \frac{V_m I_m}{2} = V_{rms} I_{rms} = VI$$

Power factor = 1 = $\cos \phi$
angle b/w V & I ↙

Power factor: Amount of power absorbed by the load.

A.C. through Inductor:

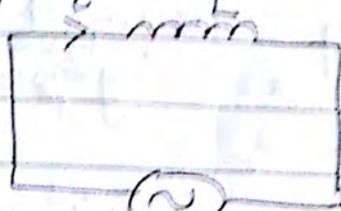

$$V = V_m \sin \omega t \quad \text{--- (1)}$$

$$V = V_m \sin \omega t \rightarrow (1)$$

$$V_m \sin \omega t = L \frac{di}{dt}$$

$$di = \frac{V_m}{L} \sin \omega t$$

$$\int di = \frac{V_m}{L} \int \sin \omega t dt$$

$$i = \frac{V_m}{\omega L} (\cos \omega t)$$

$$i = I_m (-\cos \omega t)$$


$$i = I_m \sin (\omega t - \pi/2) \rightarrow (2)$$

$$I_m = \frac{V_m}{\omega L}$$

$$\Rightarrow \frac{V_m}{I_m} = \omega L$$

$$= 2\pi f L$$

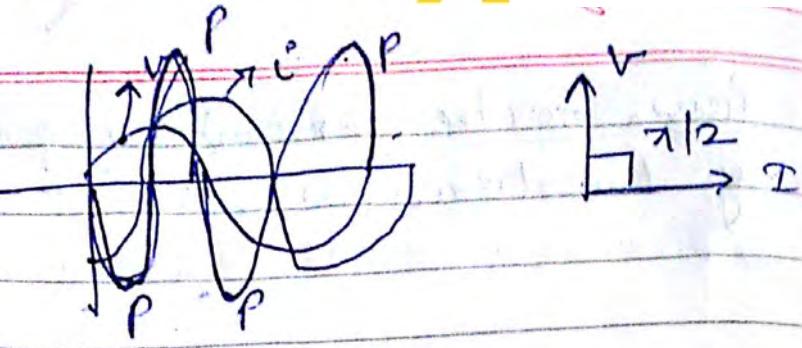$= X_L \rightarrow$ Inductive reactance
 (\rightarrow)



$$P=0$$

Energy consumed by it = 0
 $= \frac{\text{active}}{\text{avg. power}} = 0 = \text{avg. power}$


so, Reactive power will be considered

proof

$$\begin{aligned} P &= vi \\ \text{instantaneous power} &= V_m \sin \omega t \cdot I_m \sin(\omega t + \pi/2) \\ &= -V_m I_m \sin \omega t \cos \omega t \\ &= -\frac{V_m I_m}{2} \sin 2\omega t. \end{aligned}$$

$$\text{avg. power} = \frac{1}{2\pi} \int_0^{2\pi} -\frac{V_m I_m}{2} \sin 2\omega t = 0$$

A.C. through capacitance:

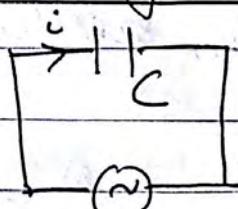

$$v = V_m \sin \omega t$$

$$v = V_m \sin \omega t \rightarrow ①$$



$$q = CV = C V_m \sin \omega t$$

$$i = \frac{dq}{dt}$$

$$i = wC V_m \cos \omega t.$$

$$= I_m \cos \omega t.$$

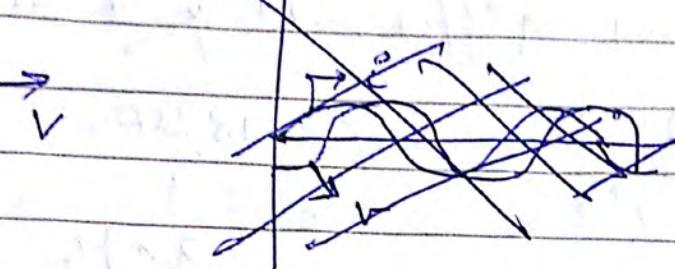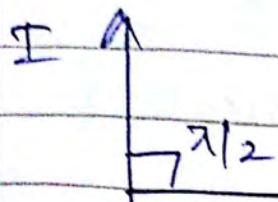
$$= I_m \sin(\omega t + \pi/2) \rightarrow \textcircled{D}$$



$$\frac{V_m}{I_m} = \frac{1}{wC}$$

$$= \frac{1}{2\pi f C}$$

$$= X_C \quad (\textcircled{2})$$

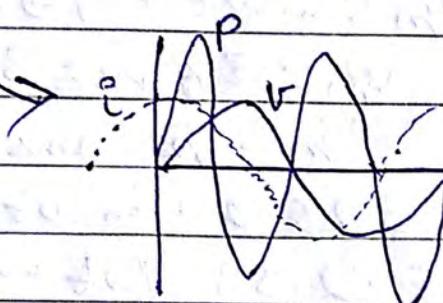

$$P = Vi$$

$$= -V_m \sin \omega t I_m \sin(\omega t + \pi/2)$$

$$= V_m I_m \sin \omega t \cos \omega t.$$

$$= \frac{V_m I_m \sin 2\omega t}{2}$$

$$\text{avg. } P = \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m \sin \omega t}{2} = 0$$

Net power absorbed in an inductor
and in capacitor is 0

Q ~~318 μF~~
~~378 μF~~ capacitor is connected across 230 V, 50 Hz. system.

- (i) Determine capacitive reactance
- (ii) rms value of current
- (iii) Freqⁿ for voltage & current

Soln:

$$C = 318 \mu F$$

$$\textcircled{1} \quad X_C = \frac{1}{2\pi f C} = 10 \Omega$$

\textcircled{2} rms value of current

$$= \frac{V}{X_C} = \frac{230}{10} = 23 A$$

\textcircled{3}

$$v = V_m \sin \omega t$$

$$i = I_m \sin(\omega t + \pi/2)$$

$$V_m = \sqrt{2} V_{rms} = 32.5 \cdot 27 V$$


$$I_m = \sqrt{2} I_{rms} = 32.53 A$$

$$v = 32.5 \cdot 27 \sin \omega t$$

$$v = 32.53 (\omega t + \pi/2)$$


17.

R-L Series A.C. Circuit:

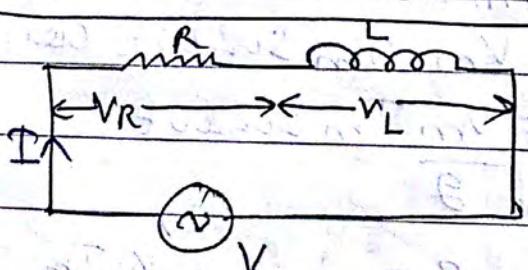

$$V_R = I R$$

$$V_L = I X_L$$

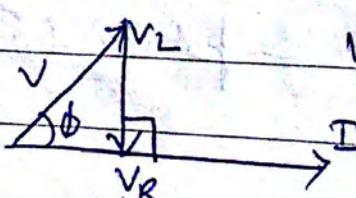

Voltage triangle

$$V = \sqrt{V_R^2 + V_L^2}$$

$$= \sqrt{(I_R)^2 + (I_X)_L^2}$$

~~$$= I \sqrt{R^2 + X_L^2}$$~~

$$V = IZ$$

$$Z = \sqrt{R^2 + X_L^2} \quad (\text{Impedance})$$

$\phi \rightarrow$ Power factor angle

$$\tan \phi = \frac{X_L}{R} \quad \frac{V_L}{V_R} = \frac{I_X L}{I R} = \frac{X_L}{R}$$

$$\cos \phi = \frac{V_R}{V} = \frac{IR}{IZ} = \frac{R}{Z}$$

(4) Admittance d^{-1}

Impedance (Z)

(X) Reactance d^{-1}

susceptance (B)

$$Y = \frac{1}{Z}, \text{ Siemens.}$$

$$P = I_m V_m \sin \omega t \sin(\omega t - \phi)$$

$$= \frac{V_m I_m}{2} [2 \sin \omega t - \sin(2\omega t - 2\phi)]$$

$$= \frac{1}{2} V_m I_m [\cos \phi - \cos(2\omega t - 2\phi)]$$

$$P = \frac{1}{2} V_m I_m \cos \phi - \frac{1}{2} V_m I_m \cos(2\omega t - 2\phi)$$

Instantaneous power

of instantaneous power = 0


Integrate instantaneous power by
Over a cycle to get avg. power

$$\text{avg. power} = \frac{1}{2} V_m I_m \cos \phi$$

$$= V_m I_m \cos \phi$$



$\frac{\sqrt{2} \times \sqrt{2}}{2}$

$$P = V I \cos \phi$$

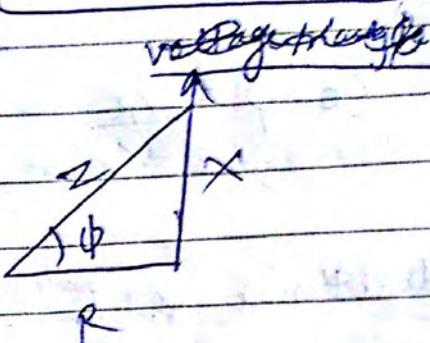

Impedance triangle

Voltage triangles:

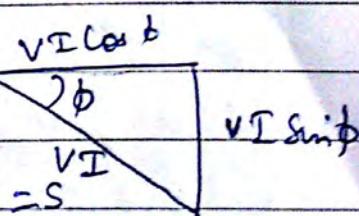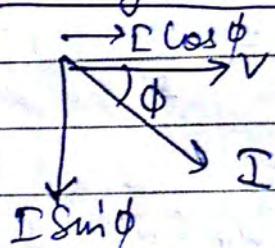

$VI \rightarrow$ Real power / active power / true power

$Q \Rightarrow$ Reactive power

$S \Rightarrow$ apparent power

or avg. power

$$S = \sqrt{P^2 + Q^2}$$

~~S → from source to load~~
~~Q → power absorbed from load~~

* Apparent Power: Total power that appears to be transferred b/w source & load ($S = VI$). [V.A → volt amp.]

* True Power: It is that power which is actually consumed in the circuit. Power is consumed in resistance only since inductor and capacitor does not consume any active power. It is useful component on apparent power.

$$P = VI \cos \phi \quad [\text{Watts}]$$


* Reactive power: Component of apparent power which is neither consumed nor does any useful work in the circuit. Circulating power is called as reactive power.

$$Q = VI \sin \phi \quad [\text{V.A.R}]$$

volt
ampere
reactive

$$\cos \phi = \frac{P}{S}$$


RC-series A.C. circuit:

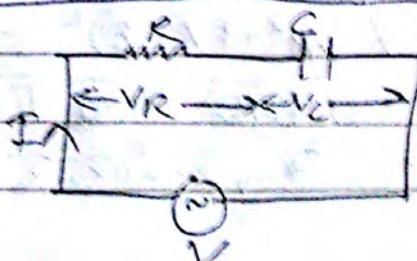


$$V_R = IR$$

$$V_C = IX_C$$

$$Z = \sqrt{R^2 + X_C^2}$$

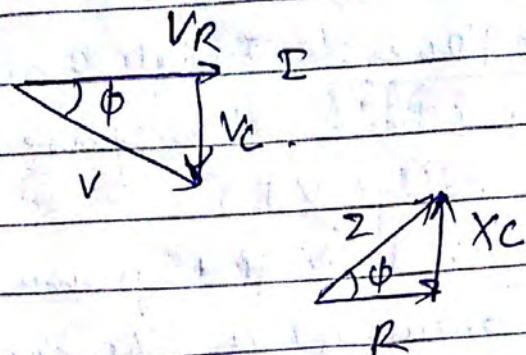



10 | 2 | 17 R-L-C Series A.C. Circuit:

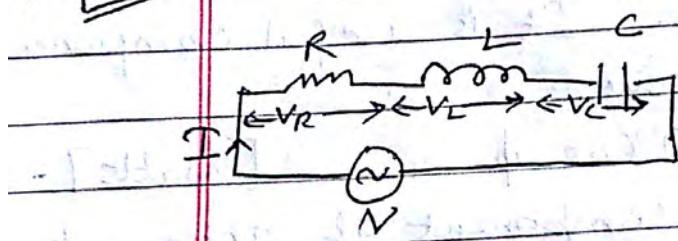

$$V_R = IR$$

$$V_L = \Sigma X_L$$

$$V_C = IX_C$$

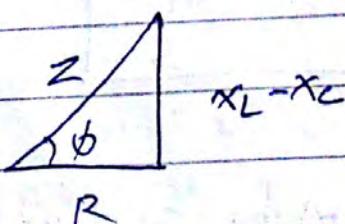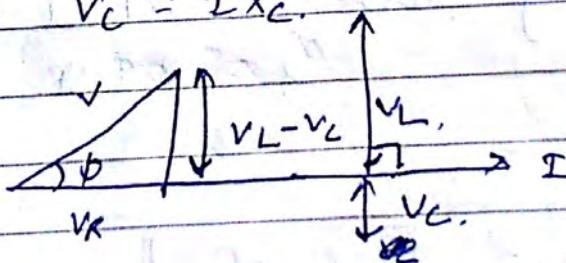

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$= \sqrt{(IR)^2 + (IX_L - IX_C)^2}$$

$$= I \sqrt{R^2 + (X_L - X_C)^2}$$

$$V = IZ$$

$$Z = \sqrt{R^2 + (x_L - x_C)^2} = \underbrace{\sqrt{R^2 + j(x_L - x_C)^2}}_{\text{check}}$$

$$\cos \phi = R/Z$$

$$\tan \phi = \frac{V_L - V_C}{R} = \frac{x_L - x_C}{R}$$

$$x_L > x_C$$

$x_L - x_C \rightarrow +iv$ I leads V by ϕ


$x_L - x_C \rightarrow -iv$ I lags V by ϕ .

$$x_L > x_C$$


$$x_L - x_C = 0$$

$(x_L = x_C)$ in phase with voltage

$Z = R$ [Resonance condition] $\phi = 0$

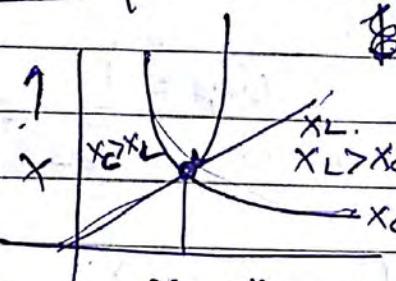

~~start decreasing~~
→ frequency

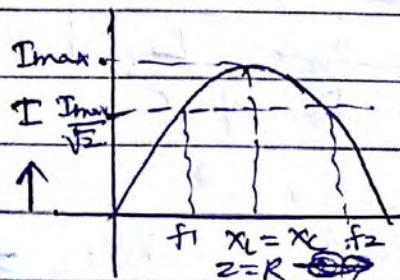


~~start decreasing~~

→ frequency \rightarrow ~~check~~

f_2

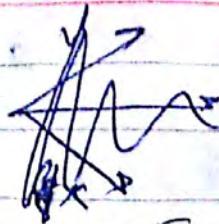Band width = $f_2 - f_1$ [lower & upper
et homogeneous
of frequency]



Resonant Frequency:

$$x_L = x_C$$

$$2\pi f L = \frac{1}{2\pi f C}$$

$$f_R = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

$$\omega_R = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$

$$Q \text{ Factor} = \frac{x_C}{R} = \frac{\omega_R L}{R}$$

$$\omega_R = \frac{1}{\sqrt{LC}}$$

$$Q \text{ factor} = \frac{x_C}{R} = \frac{1}{\omega_R C R}$$

$$Q = \frac{1}{R} \cdot \sqrt{\frac{L}{C}}$$

$$Q \text{ factor} = \frac{V_L}{V} = \frac{I X_L}{I R} = \frac{X_L}{R}$$

$$= \frac{V_C}{V} = \frac{I X_C}{I R} = \frac{X_C}{R}$$

Q-factor : Quality factor circuit.

B.W \rightarrow Band width (used in comm' networks, (radio frequency band).)

$$B.W \quad f_2 = f_0 + \frac{R}{4\pi L}$$


$$f_1 = f_0 - \frac{R}{4\pi L}$$

$$f_r = \sqrt{f_1 + f_2}$$

$$B.W = f_2 - f_1$$


~~Q10/17~~

Superposition theorem:

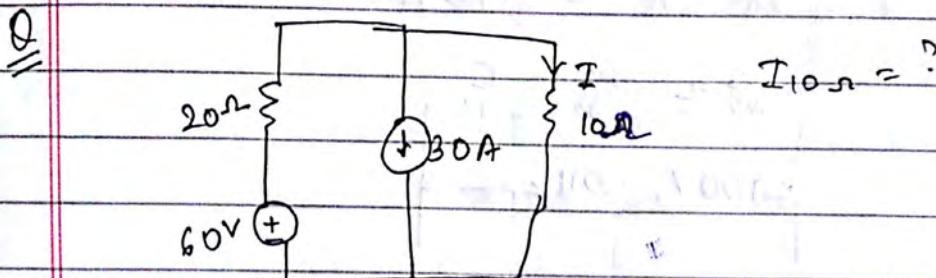


Sol'n:

Case I:

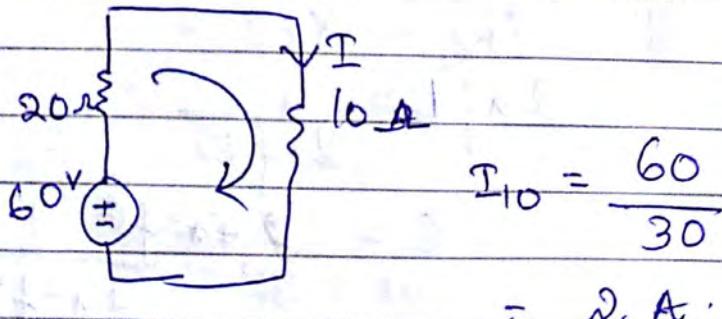

Case II:

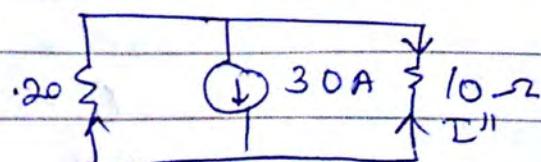

$$I'' = \frac{30 \times 20}{30} = 20A$$

$$I = .2 - 20 \\ = -18A$$

~~Q217~~


Q A circuit consists of resistance of 4Ω , Inductance 0.5 Henry , variable capacitance in series across $100V$, 50Hz supply

(i) Calculate value of capacitance to produce resonance.

(ii) Voltage across capacitance

(iii) Q factor of the circuit.

Sol'n:

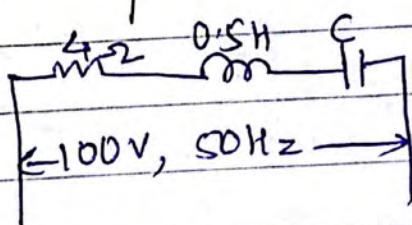

$$X_L = X_C$$

$$Z = R$$

$$I = V/R$$

$$\frac{X_L}{2\pi f L} = \frac{X_C}{2\pi f C}$$

$$C = \frac{1}{4\pi^2 f^2 L}$$

$$C = \frac{1}{4(3.14)^2 (50)^2 (0.5)}$$

$$C = \frac{1}{39438.4}$$

$$C = 20 \cdot 26 \mu F.$$

~~V = I Xc~~

$$\therefore I = \frac{100}{0.4} = 25 A.$$

$$\begin{aligned} V_c &= IX_c \\ &= \frac{25}{2 \times 3.14 \times 50 \times 20.26} \\ &= \frac{25}{6364.86} \\ &= 3.92 \times 10^{-3} V. \\ &= 3925 V. \end{aligned}$$

$$Q = \frac{\omega L}{R} = 39.27$$

Q) Coil of resistance 40Ω , $L = 0.75 H$ are connected in series. Resonant freq: $= 55 \text{ Hz}$. If supply voltage is $250V, 50 \text{ Hz}$ find line current, power factor, power consumed (active power).

Soln: $f_r = \frac{1}{2\pi\sqrt{LC}}$.

$$55 = \frac{1}{2\pi\sqrt{0.75 C}}$$

$$[C = 11.16 \mu F]$$

$$X_L = 2\pi f L = 235.6 \Omega$$

$$X_C = \frac{1}{2\pi f C} = 285.10 \Omega$$

* Always write whether ϕ is leading / lagging (power factor)

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= 83.63 \Omega$$

$$I = \frac{V}{Z} = 3.92 A$$

$$\text{Q.e } \frac{R}{Z} = \cos \phi$$


$$\therefore \phi = 0.628 \text{ rad leading}$$

$$P = V I \cos \phi$$

$$P = 617.63 W$$

$$S = V I = \sqrt{P^2 + Q^2}$$

Parallel A.C Circuit:

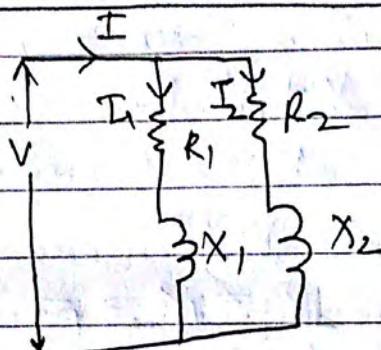

$$Z_1 = 4 + j0.5 \rightarrow \text{rectangular form}$$

$$Z = \sqrt{4^2 + (0.5)^2} < \tan^{-1}\left(\frac{X}{R}\right)$$

Polar form

$$Z = M < \theta$$

$$M_1 < \theta_1$$

$$M_2 < \theta_2$$

$$M_1 M_2 < \theta_1 + \theta_2$$

$$\frac{M_1}{M_2} < \theta_1 - \theta_2$$

$$a + j b = m \angle \theta \\ = \sqrt{a^2 + b^2} \angle \tan^{-1}(b/a)$$

$$M(\cos \theta + j \sin \theta) = M \angle \theta \\ (\text{rectangular form})$$

$$I = I_1 + I_2$$

$$= \frac{V}{Z_1} + \frac{V}{Z_2} = V \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right)$$

$$= V \left(\frac{Z_1 + Z_2}{Z_1 Z_2} \right).$$

$$I = V Y_1 + V Y_2. \quad \frac{1}{Z_1} = Y_1 \\ = V(Y_1 + Y_2).$$

$Y \rightarrow$ Conductance admittance $\frac{1}{Z_2} = V_2$

$$I_{-} = V Y_{-}$$

$$Z = \frac{1}{2S \angle \theta}$$


$\angle \theta \rightarrow$ at angle θ

$$Y = \frac{1}{2S} \angle (-\theta)$$

$$Z = \frac{1}{2S \theta + j 0.5}$$

$Y =$ (Relate to above & then reciprocate.)

3/3/17

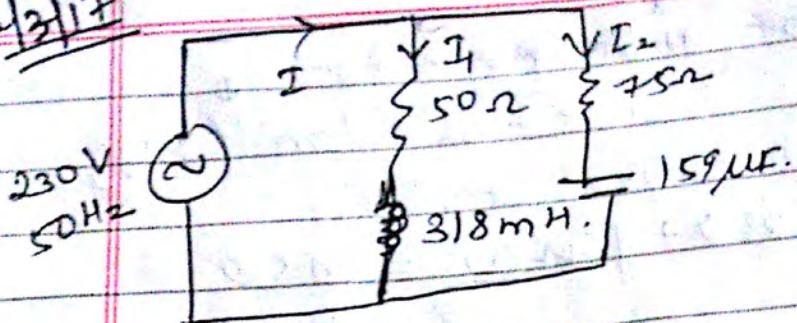

Determine supply current & circuit power factor.

Soln:

$$\text{①. } I = I_1 + I_2$$

$$= \frac{V}{Z_1} + \frac{V}{Z_2}$$

$$I = V \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right)$$

$$I = I_1 + I_2$$

$$= \frac{V}{Z_1} + \frac{V}{Z_2}$$

$$= V(Y_1 + Y_2)$$

$$I = VY$$

$$Y = Y_1 + Y_2$$

$$Z_1 = R_1 + jX_L$$

$$= 50 + j(318 \times 10^{-3})$$

$$= 50 + j(2\pi f(318 \times 10^{-3}))$$

$$Z_2 = R_2 - jX_C$$

$$= 75 - j(159 \times 10^{-6})$$

$$= 75 - j\left(\frac{1}{\omega C}\right)$$

$$= 75 - j\left(\frac{1}{2\pi f \times 159 \times 10^{-6}}\right)$$

$$Z_1 = 50 + j(99.99) \Omega$$

$$Z_2 = 75 - j(20.01) \Omega$$


$$I \text{ (in polar form)} \rightarrow 3.92 \angle -15^\circ$$

-ive sign means current is lagging

$$\text{Power factor} = \frac{\cos}{\sim} (-15^\circ) \text{ (Degree)}$$

$$= 0.962 \text{ (lagging)}$$

Resonance in parallel A.C. circuit:

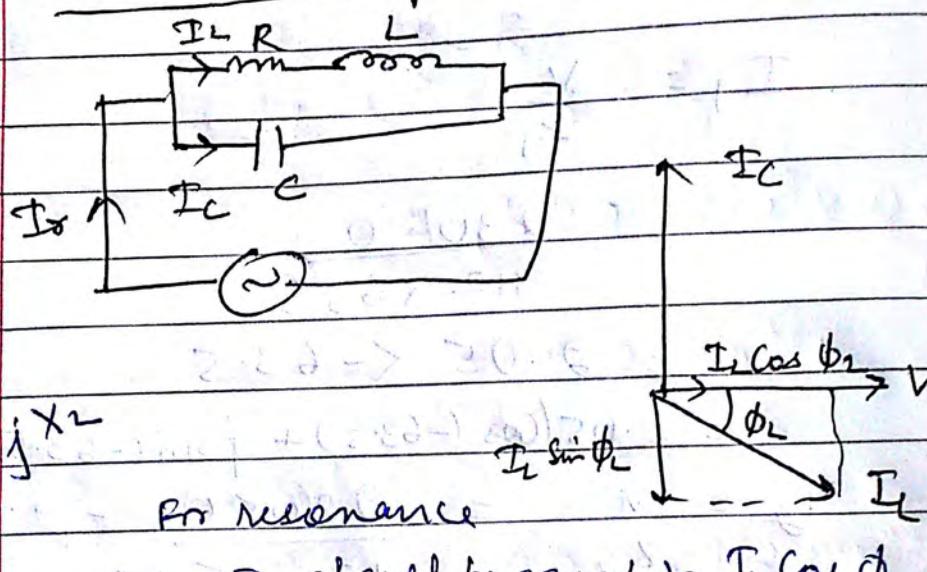


For resonance

$\Rightarrow I$ should be equal to $I_L \cos \phi_L$

$$\therefore I_C - I_L \sin \phi_L = 0$$

$$I_C = I_L \sin \phi_L$$

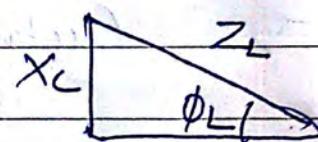

$$\frac{V}{X_C} = \frac{V}{Z_L} \left(\frac{X_L}{Z_L} \right)$$

$$\text{or } X_L X_C = Z_L^2$$

$$\omega L / \omega C = Z_L^2$$

$$\frac{L}{C} = R^2 + (2\pi f_r)^2$$

$$(2\pi f_r L)^2 = \frac{L}{C} - R^2$$

$$2\pi f_r L = \sqrt{\frac{L}{C} - R^2}$$

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

Impedance at resonance:

$$I_r = I_L \cos \phi_L$$

$$\frac{V}{Z_r} = \frac{V}{Z_L} \frac{R}{Z_L}$$

$$\frac{1}{Z_r} = \frac{R}{Z_L^2}$$

$$Z_L^2 = \frac{L}{C}$$

$$\rightarrow \frac{1}{Z_r} = \frac{R}{Z_L^2} = \frac{RC}{L}$$

~~$$Z_d = \frac{1}{Z_r}$$~~

$$Z_d = \frac{1}{CR}$$


dynamic Impedance.

- Q) Dynamic impedance of 11 resonant circuit is 500 k Ω . Circuit consists of 250 pF capacitor in 11 with coil of res = 10 Ω . Calculate
- coil inductance
 - resonant frequency.

(iii) B-factor

Soln:
(1)

$$Z_L = 500 \text{ k}\Omega$$

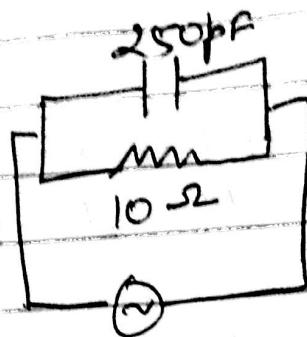

$$Z_L = \frac{L}{CR}$$

$$L = Z_L CR$$

$$= (500) \times 10^3 \times 10 \times 250 \times 10^{-12}$$

$$= 1.25 \times 10^{-3} \text{ H}$$


$$(i) f_r = \frac{1}{2\pi} \sqrt{\frac{1}{(1.25 \times 10^{-3})(250 \times 10^{-3})}} \quad (1.25 \times 10^{-3})$$

$$= \frac{1}{2\pi \sqrt{}}$$


1/3/17

3 phases Systems: Module IV

Generation of polyphase supply:

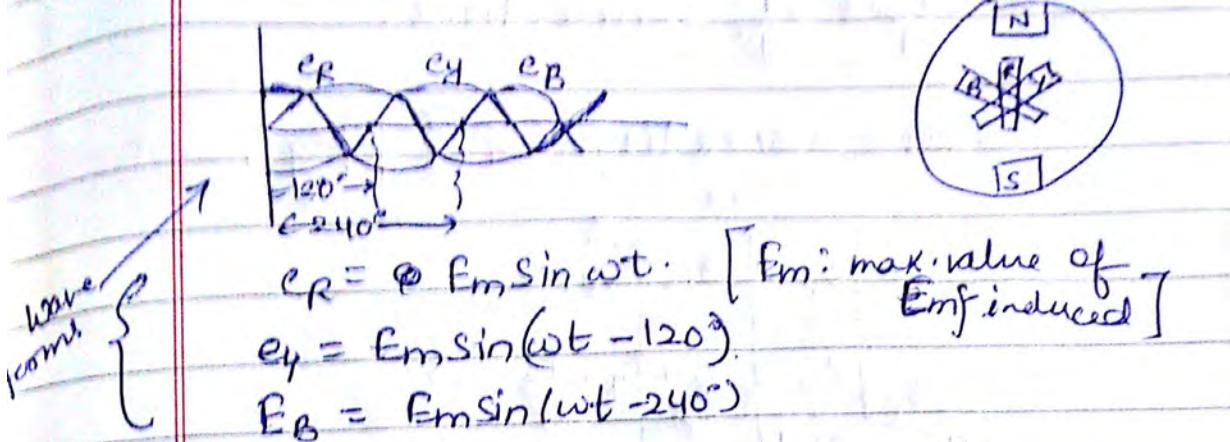

Phasor diag:

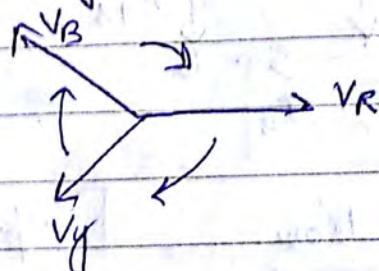

* Power delivered by 3 phase is more
(3 Times $VI \cos \phi$) Power factor is better.

Advantages of 3 phase:


- ① Power delivered by 3 phase is more
- ② Lesser conductor for transmission of same output of power at same voltage
- ③ Polyphase motors have uniform torque whereas it is pure pulsating in single phase
- ④ Power factor of single phase machine is ~~more~~ ^{lower} than 3 phase machine

(4) Efficiency of 3 phase machine is higher than single phase machine.




2 types of connections:

Star Connection: [Supply]

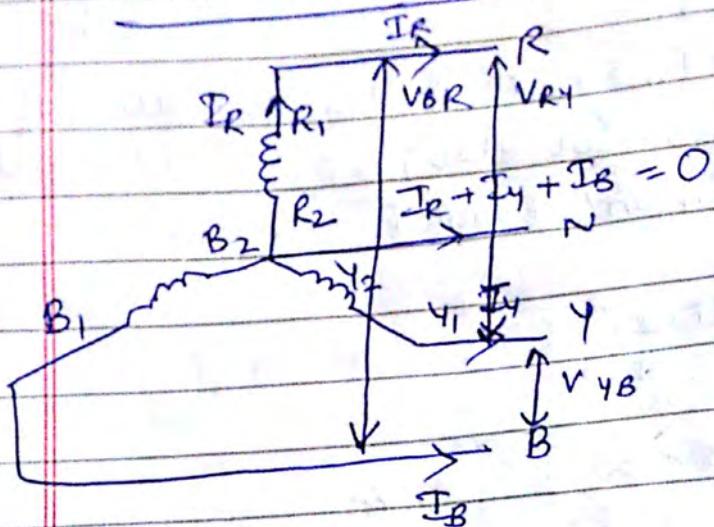

Delta connection: [Supply].

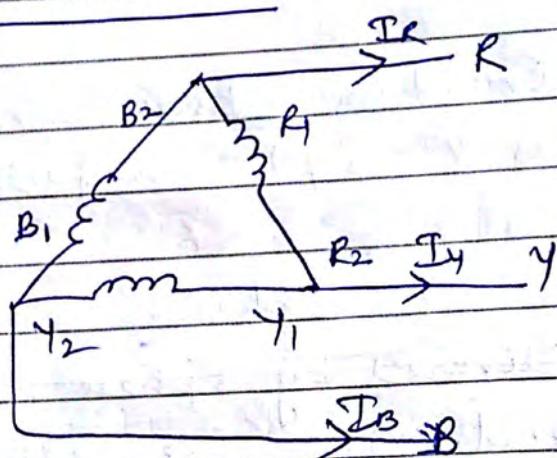

* NO neutral pt. in Delta connection

* Phase seq.: sequence at which each phase reaches its max. value
(General RYB)

↳ due to this direction of torque can be changed



If Voltage is measured b/w
2 lines which
are line voltages
(V_{RY} , V_{YB} , V_{RB})


* Phase voltage: Voltage b/w each phase
(voltage b/w 1 line & neutral)

* In star connection: line current =
= phase current
but line voltage \neq phase voltage


* In delta connection: every phase is
connected b/w 2 lines so line voltage
= phase voltage but line
current \neq phase current

In star connection:
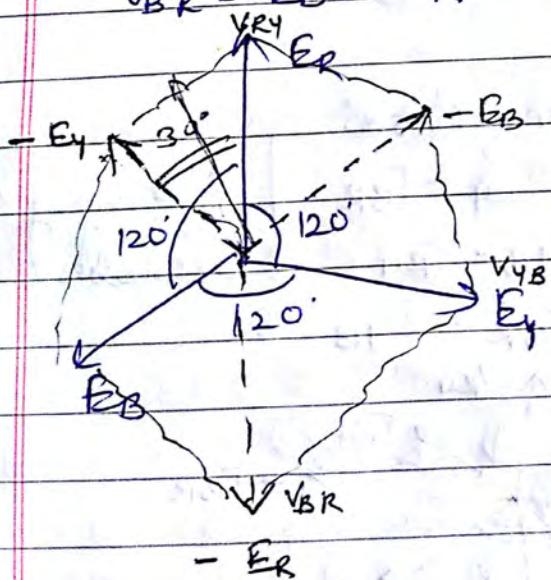
$$\begin{aligned} V_{RY} &= E_R - E_Y \\ V_{YB} &= E_Y - E_B \\ V_{BR} &= E_B - E_R \end{aligned} \quad \left. \begin{array}{l} \text{phase voltage in} \\ \text{terms of line} \\ \text{voltages} \end{array} \right\}$$



Apply
KCL law to
obtain
relation

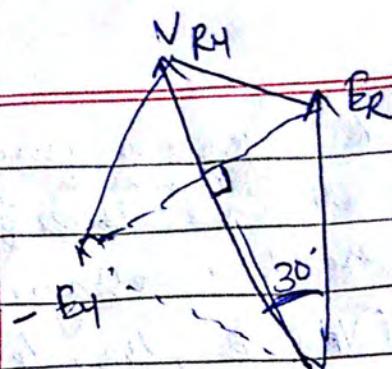

$$V_{RY} = 2 E_R \cos 60^\circ (60)_2.$$

$$= 2 E_R \frac{\sqrt{3}}{2}$$

$$V_{RY} = \sqrt{3} E_R$$

$$V_L = \sqrt{3} V_{\text{phase}}$$

$$I_L = I_{\text{phase}}$$

$$P = 3 V_{\text{phase}} I_{\text{phase}} \cos \phi.$$

$$= 3 \frac{V_L}{\sqrt{3}} I_L \cos \phi.$$

$$P = \sqrt{3} V_L I_L \cos \phi$$


* In Delta connection:

$$I_R = I_{RY} - I_{BR}$$

$$I_Y = I_{YB} - I_{RY}$$

$$I_B = I_{BR} - I_{YB}$$

[Applying KCL
at nodes]

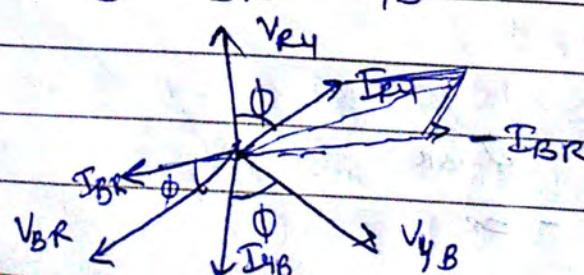

I_{ph} → phase current

I_L → line current

angle b/w ΔV_{ph} & $I_R \rightarrow 30^\circ + \phi$

$$I_R = 2 I_{ph} \cos 30^\circ \\ = 2 I_{ph} \frac{\sqrt{3}}{2}$$

$$I_R = \sqrt{3} I_{ph}$$


$$I_L = \sqrt{3} I_{phase}$$

$$V_L = V_{phase}$$

8/3/17

Q 3 coils each having res. of 20Ω and inductive reactance 15Ω are connected in star to $400V$, 3-phase $50Hz$ supply. Calculate line current, power factor & power supplied.

Sol:

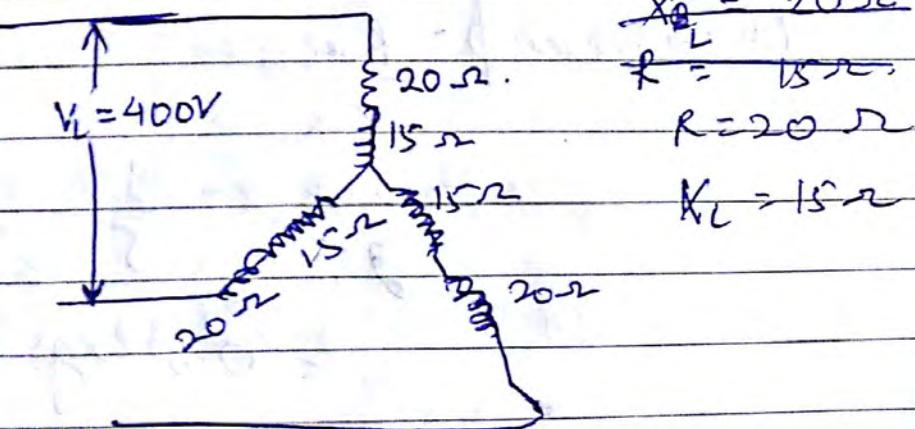

Phase B

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} \quad \Rightarrow \quad V_{ph} = 400V$$

$$V_{ph} = \frac{V_L}{\sqrt{3}}$$

$$= \frac{400}{\sqrt{3}}$$

$$V_{ph} = 231V$$

$$Z_{ph} = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{(20)^2 + (15)^2}$$

$$= \sqrt{400 + 225}$$

$$= \sqrt{625}$$

$$= 25 \Omega$$

$$I_{ph} = \frac{231}{25} = 9.24 A = I_L$$

Power factor

$$\text{Power factor} \cos \phi = \frac{R_{ph}}{Z_{ph}}$$

$$= \frac{20}{25} = \frac{4}{5}$$

= 0.8 lag

$$\text{Power} = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} V_{ph} I_{ph} \cos \phi$$

$$= \sqrt{3} \times 0.8 \times 9.24 \times 231 = 5121W$$

Q) 3 similar coils, $R = 5\Omega$, $X_L = 0.02\text{H}$
 are connected in delta. to 240V ,
 3 phase 50 Hz, supply. Calculate
 line current & total power absorbed.

Soln:

$$V_L = 440\text{V}$$

$$R = 5\Omega$$

$$X_L = 0.02\text{H}$$

$$f_L = 50\text{Hz}$$

(i) Delta:

$$\text{Ans} V_L = V_{\text{phase}}$$

$$V = IR$$

$$I_{ph} = \frac{V_{ph}}{Z} \quad \text{Ans}$$

$$= \frac{240}{\sqrt{(5)^2 + (0.02)^2}} \quad \text{Ans}$$

$$= 88 \text{ A}$$

$$\Rightarrow \cancel{440} \\ \cancel{\sqrt{25 + 0.0004}}$$

$$Z = \sqrt{(5)^2 + (2\pi(50)(0.02))}$$

$$= \sqrt{25 + (0.0002\pi)}$$

$$= \sqrt{25 + 2\pi}$$

$$= 8.05\Omega$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{440}{8.05} = 54.6A$$

$$I_L = \sqrt{3} I_{ph}$$

$$I_L = 95.02A$$

$$P = VI \cos \phi$$

$$\cos \phi = \frac{R_{ph}}{Z_{ph}}$$

$$\cos \phi = -0.62$$

$$P = 3V_{ph} I_{ph} \cos \phi = 45kW$$

Star Connection:

$$I_L = 54.6A = I_{ph}$$

$$V_L = \sqrt{3} V_{ph}$$

~~$\frac{V_{ph}}{\sqrt{3}}$~~ $\approx V_{ph} =$

~~$P = \sqrt{3} V_L I_L \cos \phi$~~

$$= \sqrt{3}(440)(54.6)(0.8)$$

~~$= 33288.630W$~~

~~$= 33288.6kW$~~

$$15kW$$

lagging $\rightarrow R_L$
leading $\rightarrow R_C$

$$\text{React. in power} = \sqrt{3} V_L I \sin \phi$$

$$\text{Active} \quad S = \sqrt{3} V_L I$$

Q A Balanced (impedances are same) delta connected load takes a line current of 18A at power factor of ~~0.85~~ 0.85 leading from 400V, 3 phase 50Hz supply. Calculate res- & capacitance of each branch of load.

Soln:

~~$V_L = 400V$~~

~~$\cos \phi = 0.85$~~

~~$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{400}{\cancel{Z_{ph}}} = 0.12$~~

~~$I_L = \sqrt{3} V_{ph} I_{ph}$~~

Delta connected load,

~~$I_L = \sqrt{3} I_p \quad , \quad V_L = V_{ph}$~~

$$I_{ph} = \frac{I_L}{\sqrt{3}}$$

$$= \frac{18}{\sqrt{3}}$$

$$= 10.37 \text{ A.}$$

$$\cos \phi = 0.85 \text{ Leading} = \frac{R_{ph}}{Z_{ph}}$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{400}{10.37} = 38.5 \Omega$$

$$R_{ph} = R_B - (38.5)(0.85)$$
 ~~$= 32.72 \Omega$~~

Z_{ph}

$$R_{ph} = Z_{ph} \times \cos \phi$$

$$= 32.72 \Omega$$

$$Z_{ph} = \sqrt{R^2 + X_C^2}$$

$$38.5 = \sqrt{(32.72)^2 + X_C^2}$$


$$X_C = 20.99 \Omega$$



$$X_C = \frac{1}{2\pi f C}$$

$$C = 156.9 \mu F$$

$X_L - X_C \rightarrow$ net reactance


Measurement of power in 3 phase circuit:

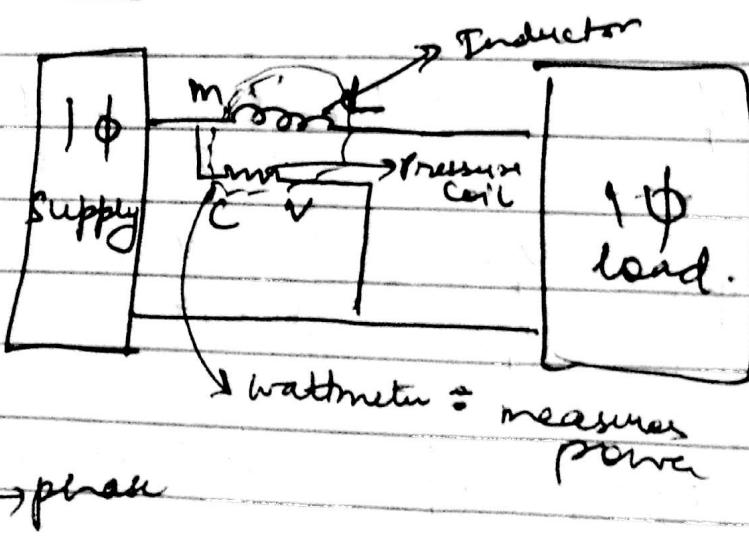

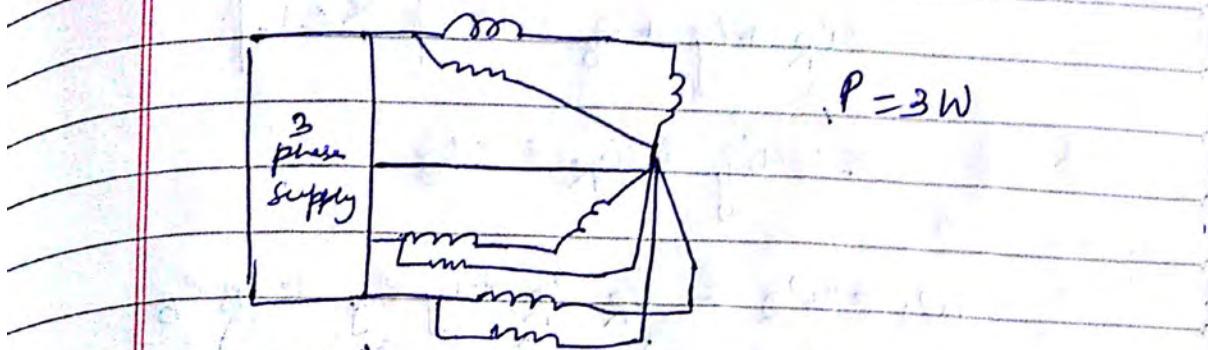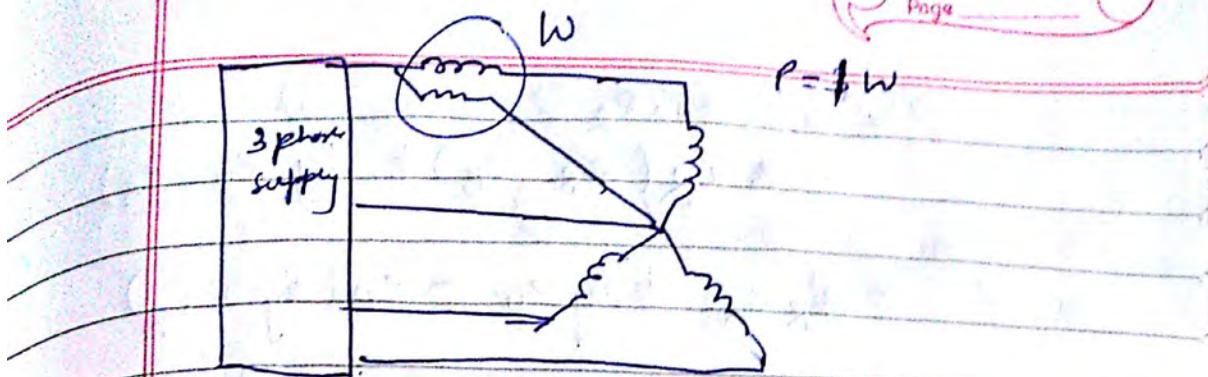

~~1st & 17 Deriv not sub always come.~~

Two Wattmeter Method:

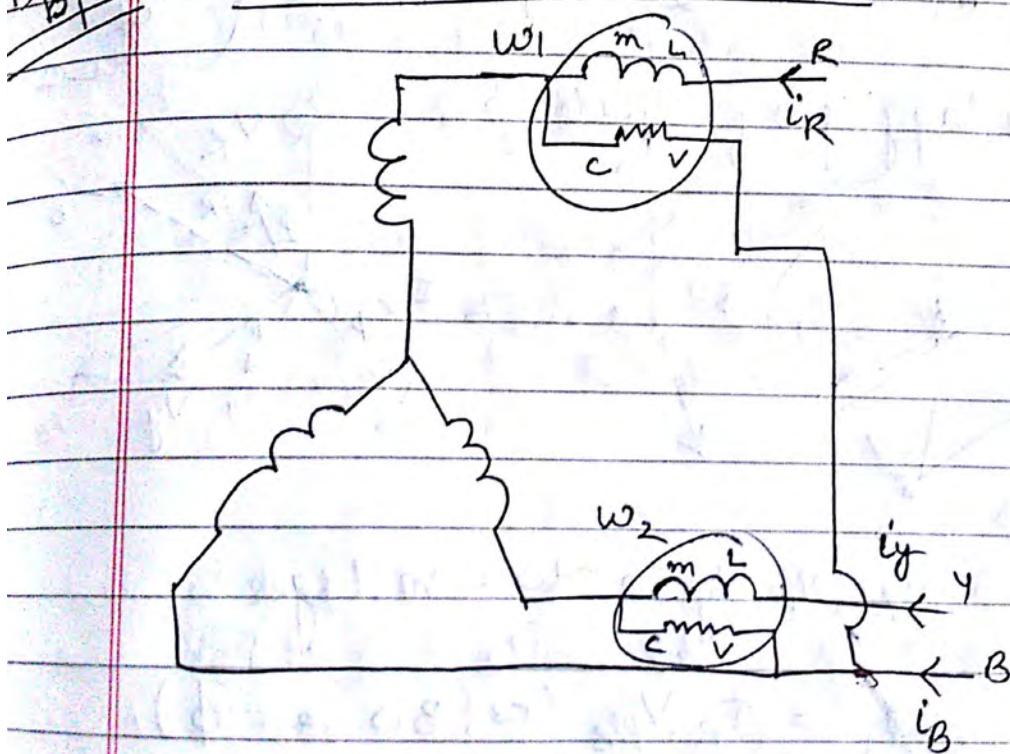

$$W_1 = i_R \{ e_R - e_B \}$$

↓ ↴
current find potential
coil (higher - lower potential)

$$W_2 = i_Y \{ e_Y - e_B \}$$

$$P = W_1 + W_2$$

$$P = w_1 + w_2 \\ = \epsilon_R i_R (\epsilon_R - \epsilon_B) + i_y (\epsilon_y - \epsilon_B)$$

$$= i_R \epsilon_R + i_y \epsilon_y - \epsilon_B (i_y + i_R)$$


$$i_R + i_y + i_B = 0 \quad [KCL]$$

$$\therefore i_y + i_R = -i_B$$

$$w_1 + w_2 = i_R \underbrace{\epsilon_R}_{P_R} + i_y \underbrace{\epsilon_y}_{P_Y} + \underbrace{i_B \epsilon_B}_{P_B}$$

$$\therefore w_1 + w_2 = P_Y + P_B + P_R \quad (\text{Total power of load})$$

current is lagging by angle ϕ

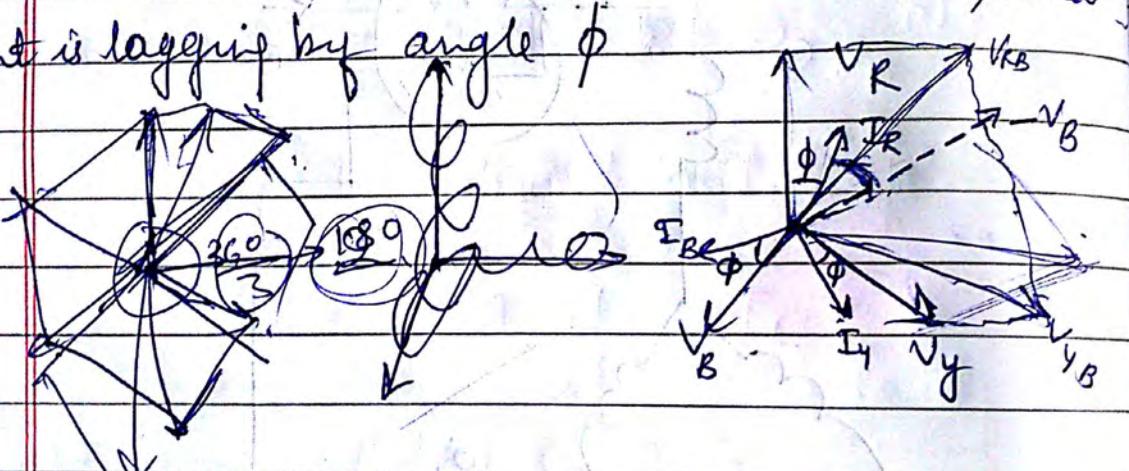

$V_R, V_B, V_Y \rightarrow$ phase voltages

$$w_1 = I_R V_{RB} \cos(30^\circ - \phi)$$

$$w_2 = I_Y V_{YB} \cos(30^\circ + \phi)$$

load is balanced,

$$|I_R| = |I_Y| = |I_B| = I_c$$

$$|V_{xy}| = |V_{yz}| = |V_{Bd}| \div V_L$$

$$\omega_1 = V_L I_L \cos(30 - \phi)$$

$$\omega_2 = V_L I_L \cos(30 + \phi).$$

$$\rho = \omega_1 + \omega_2$$

$$= V_L I_L [\cos(30 - \phi) + \cos(30 + \phi)]$$

$$= V_L I_L [\cos 30 \cos \phi + \sin 30 \sin \phi + (\cos 30 \cos \phi - \sin 30 \sin \phi)]$$

$$= V_L I_L (2 \cos 30 \cos \phi)$$

$$= V_L I_L \times 2 \times \frac{\sqrt{3}}{2} \cos \phi.$$

$$[\omega_1 + \omega_2 = \sqrt{3} V_L I_L \cos \phi] \rightarrow ①$$

Similarly

$$[\omega_1 - \omega_2 = V_L I_L \sin \phi] \rightarrow ②$$

$$\tan \phi = \sqrt{3} \left(\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right)$$

$$\therefore \phi = \tan^{-1} \left(\sqrt{3} \left(\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right) \right)$$

$$\rho f = \cos \phi$$

$$= \cos \left(\tan^{-1} \left(\sqrt{3} \left(\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right) \right) \right)$$

$$\text{If } \omega_1 = \omega_2 = 0.$$

① If $\phi = 0$ ($\omega_1 = \omega_2$)
 P.F = 1 (unity)
 $\omega_1 = \omega_2 = \frac{\omega}{2}$

② If P.F = 0.5, $\phi = 60^\circ$

$$\omega_1 = \frac{\sqrt{3}}{2} V_L I_L$$

$$\omega_2 = 0.$$

③ $\phi = 90^\circ$, P.F = 0.785 = 0.8
 $\omega_1 = \phi - \omega_2$

$$\omega_1 = \frac{1}{2} V_L I_L$$

$$\omega_2 = \frac{1}{2} V_L I_L$$

20/3/17

Q) 2 wattmeters are connected to measure input of 15 H.P, 50Hz, 3 phase induction motor at full load. Full load efficiency and power factor are 0.9 and 0.8 respectively. Find readings of 2 wattmeters.

Soln: Power = 15 H.P
 $= 15 \times 746$
 $= 11190 \text{ W}$

aminotes

$$\cos \phi = \cos \left[\tan^{-1} \left(\frac{w_1}{w_2} \right) \right]$$

$$\eta = \frac{O/P}{I/P} = \frac{15 \times 746}{I/P} = 0.9.$$

$$P_{ui} = 12433.3 \text{ W}.$$

$$P_{ui} = \sqrt{3} V_L I_L \cos \phi.$$

$$w_1 = V_L I_L \cos(30 - \phi) = 8783.17 \text{ W}$$

$$w_2 = V_L I_L \cos(30 + \phi) = 3476 \cdot 569 \text{ W}$$

$$V_L I_L = 8972 \text{ A}$$

Q for a certain load 1 of the wattmeter read 20 kW and other 5 kW. After the voltage circuit transformer wall has been reversed. Calculate power and power factor of the load.

$$w_1 = 20 \text{ kW}$$

$$w_2 = -5 \text{ kW}$$

$$P = w_1 + (w_2)$$

$$= 20 - 5$$

$$P = 15 \text{ kW}$$

46.09

$$P = V_L I_L \cos \phi$$

Power factor: $\cos \phi = \cos \left[\tan^{-1} \frac{\sqrt{3} (15)}{(25)} \right]$.

$$= \cos \left[\tan^{-1} (1.039) \right].$$

$$= 0.693 (0.3273)$$

Module 2

(1)
(2)

Transformers
D.C. machines

motor

generator.

Transformer

(1) Core type of transform.



Primary winding

N_1 no. of turns in $N_2 \rightarrow$ no. of turns in

Secondary winding

Flux is generated ^{primary} by passing current in primary & secondary winding

$$e = -\frac{d\phi}{dt}$$

$$e = -N \frac{d\phi}{dt}$$

If secondary winding is open

$$I_2 = 0$$

If secondary winding is connected to load,

$$V_2 = E_2 - I_2 Z_2$$

$$\rightarrow I_2 = 0 \text{ [no load]}$$

$$V_2 = E_2$$

E_2 : due to mutual induction

E_2 : due to self induction


If $N_2 > N_1 \rightarrow$ step up transformer

$N_2 < N_1 \rightarrow$ step down transformer

$N_2 = N_1 \rightarrow$ no power

Transformer Used for isolating ~~g~~ circuit

② Shell type of transformer:

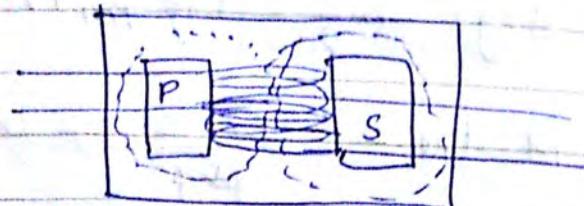

It is used to have 0 leakage flux and



Core type of transformer


1. Winding encircles the core
2. Construction is preferred for low voltage
3. Cooling is better
4. Maintenance is easy

Shell type transf.

1. Core encircles winding most part of n
2. Construction is high voltage application
3. Cooling is poor.
4. Maintenance is difficult.

Bmf equation of Transformer

~~Bm~~ ~~Phi m~~

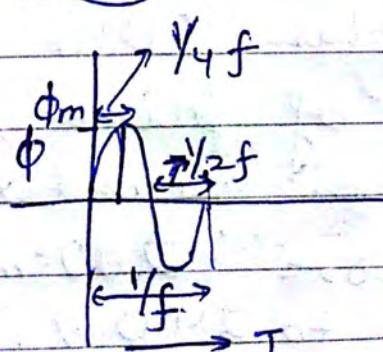

e = change in flux

$$= \frac{\text{Time}}{\frac{\Phi_m - 0}{1/4f}} = \cancel{\frac{\Phi_m - 0}{1/4f}}$$

Avg. emf / turn = $4 f \phi_m$
 Avg. emf = $4 f \phi_m N$

Form factor = $\frac{V_{rms}}{avg}$ = 1.11

$$V_{rms} \cdot emf = 4.44 f \phi_m N$$

$N_1 \rightarrow$ primary winding (no. of turns)

$N_2 \rightarrow$ no. of turns of secondary
winding

$$E_1 = 4.44 f \phi N_1$$

$$E_2 = 4.44 f \phi N_2$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = K = \text{Turns ratio of transformer}$$

Q Single phase 50 Hz transformer has 80 turns of primary winding and 400 turns on secondary winding.

Area of core : 200 cm^2 . Primary is connected to 240 V, 50 Hz supply

(i) Determine emf induced in secondary winding

(ii) Max. value of flux density in the core.

$$\rightarrow \phi/A$$

coil "N"

$$N_1 = 80$$

$$N_2 = 400$$

$$\Delta = \frac{N_2 \phi}{a}$$

$$= (400 - 80)$$

$$E_1 = 240 \text{ V.}$$

$$a = 2000 \text{ cm}^2.$$

$$K = \frac{N_2}{N_1} = \frac{E_2}{E_1}$$

$$E_2 = 240 \times 5 = 1200 \text{ V.}$$

$$E_2 = 4.44 \times 50 \times \phi_m \times N_2$$

$$\phi_m = 0.0135 \text{ wb.}$$

$$B_m = \frac{\phi}{a} = 6.75 \text{ wb/m}^2$$

→ Transformer rating is given as kVA, VA.
~~VA~~

Ideal transformer : $\text{D/P KVA} = \text{O/P KVA}$

$$V_1 I_1 = V_2 I_2$$

$$\frac{V_2}{V_1} = \frac{I_1}{I_2} = K$$

$$K = \frac{N_2}{N_1} = \frac{E_2}{E_1}$$

Turn's ratio / Transformation ratio